

EHB 211E: Basics of Electrical Circuits

Circuit Theorems

Asst. Prof. Ahmet Can Erten
(aerten@itu.edu.tr)

TA: Merve Gulle (gullem@itu.edu.tr)

1


Mesh Analysis

Mesh analysis provides another general procedure for analyzing circuits, using mesh currents as the circuit variable.

- > nodal analysis applied KCL to find unknown voltages
- > mesh analysis applies KVL to find unknown currents
- mesh analysis is only applicable to PLANAR circuits!

STEPS:

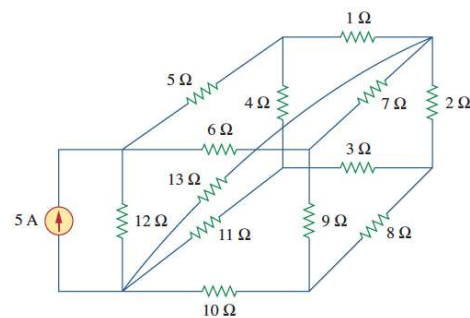1. Assign mesh currents i_1, i_2, \dots, i_n to the n meshes
2. Apply KVL to all meshes. Use Ohm's law to express voltages in terms of mesh currents
3. Solve the resulting n simultaneous equations to get mesh currents



Non-planar circuit: A circuit that can not be drawn on a single planar surface, without branches crossing each other.


EHB 211E

2

2

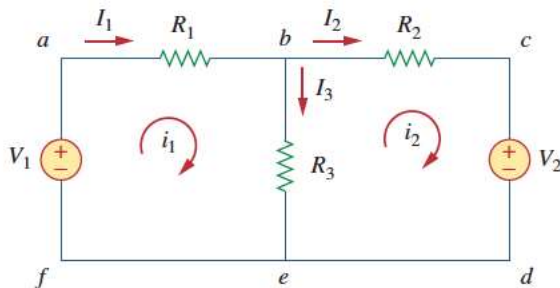Exercise

Find mesh and branch currents for the below circuit



$$I_1 = i_1, \quad I_2 = i_2, \quad I_3 = i_1 - i_2$$

KVL for each mesh:

$$\begin{aligned} -V_1 + R_1 i_1 + R_3(i_1 - i_2) &= 0 \\ (R_1 + R_3)i_1 - R_3 i_2 &= V_1 \quad (1) \end{aligned}$$

$$\begin{aligned} R_2 i_2 + V_2 + R_3(i_2 - i_1) &= 0 \\ -R_3 i_1 + (R_2 + R_3)i_2 &= -V_2 \quad (2) \end{aligned}$$

2 equations, 2 unknowns

$$\begin{bmatrix} R_1 + R_3 & -R_3 \\ -R_3 & R_2 + R_3 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} V_1 \\ -V_2 \end{bmatrix}$$


EHB 211E

3

3

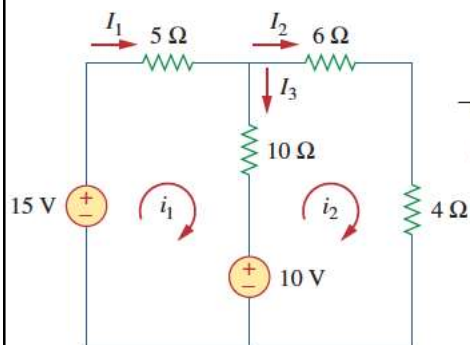Exercise

Find mesh and branch currents for the below circuit



KVL mesh 1:

$$\begin{aligned} -15 + 5i_1 + 10(i_1 - i_2) + 10 &= 0 \\ 3i_1 - 2i_2 &= 1 \end{aligned}$$

KVL mesh 2:

$$\begin{aligned} 6i_2 + 4i_2 + 10(i_2 - i_1) - 10 &= 0 \\ i_1 &= 2i_2 - 1 \end{aligned}$$

$$i_1 = 1 \text{ A}, \quad i_2 = 1 \text{ A}$$

$$I_1 = i_1 = 1 \text{ A}, \quad I_2 = i_2 = 1 \text{ A}, \quad I_3 = i_1 - i_2 = 0$$


EHB 211E

4

4

Exercise

Find mesh currents for the below circuit

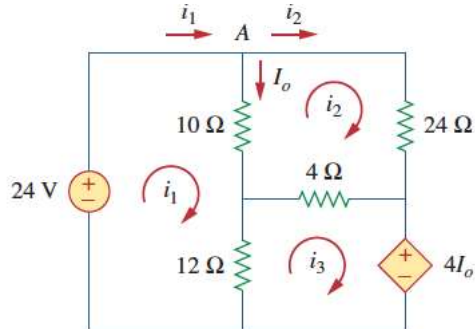

KVL mesh 1:

$$-24 + 10(i_1 - i_2) + 12(i_1 - i_3) = 0$$

$$11i_1 - 5i_2 - 6i_3 = 12$$

KVL mesh 2:

$$24i_2 + 4(i_2 - i_3) + 10(i_2 - i_1) = 0$$

$$-5i_1 + 19i_2 - 2i_3 = 0$$

KVL mesh 3:

$$4I_o + 12(i_3 - i_1) + 4(i_3 - i_2) = 0$$

at node A, $I_o = i_1 - i_2$

$$4(i_1 - i_2) + 12(i_3 - i_1) + 4(i_3 - i_2) = 0$$

$$-i_1 - i_2 + 2i_3 = 0$$

$$\begin{bmatrix} 11 & -5 & -6 \\ -5 & 19 & -2 \\ -1 & -1 & 2 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} = \begin{bmatrix} 12 \\ 0 \\ 0 \end{bmatrix}$$

3 equations, 3 unknowns

EHB 211E

5

5

Solving 3 equations using Cramer's rule:

$$\begin{bmatrix} 11 & -5 & -6 \\ -5 & 19 & -2 \\ -1 & -1 & 2 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} = \begin{bmatrix} 12 \\ 0 \\ 0 \end{bmatrix}$$

Obtain determinant

$$\Delta = \begin{vmatrix} 11 & -5 & -6 \\ -5 & 19 & -2 \\ -1 & -1 & 2 \end{vmatrix} = \begin{vmatrix} 11 & -5 & -6 \\ -5 & 19 & -2 \\ -1 & -1 & 2 \end{vmatrix}$$

$$= 418 - 30 - 10 - 114 - 22 - 50 = 192$$

$$i_1 = \frac{\Delta_1}{\Delta} = \frac{432}{192} = 2.25 \text{ A}, \quad i_2 = \frac{\Delta_2}{\Delta} = \frac{144}{192} = 0.75 \text{ A}$$

$$i_3 = \frac{\Delta_3}{\Delta} = \frac{288}{192} = 1.5 \text{ A}$$

$$\Delta_1 = \begin{vmatrix} 12 & -5 & -6 \\ 0 & 19 & -2 \\ 0 & -1 & 2 \end{vmatrix} = 456 - 24 = 432$$

$$\Delta_2 = \begin{vmatrix} 11 & 12 & -6 \\ -5 & 0 & -2 \\ -1 & 0 & 2 \end{vmatrix} = 24 + 120 = 144$$

$$\Delta_3 = \begin{vmatrix} 11 & -5 & 12 \\ -5 & 19 & 0 \\ -1 & -1 & 0 \end{vmatrix} = 60 + 228 = 288$$

EHB 211E


6

6

Mesh Analysis with Current Sources

CASE 1:

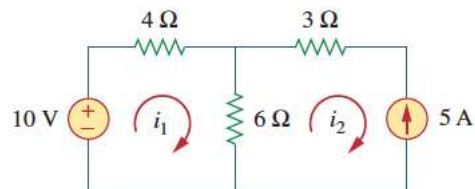When a current source exists only in one mesh:




$$i_2 = -5 \text{ A}$$

$$\begin{aligned} -10 + 4i_1 + 6(i_1 - i_2) &= 0 \\ \Rightarrow i_1 &= -2 \text{ A} \end{aligned}$$

CASE 2:

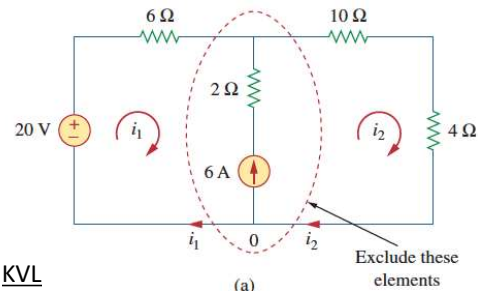When a current source exists between two meshes (supermesh!):



KVL

$$-20 + 6i_1 + 10i_2 + 4i_2 = 0$$

$$6i_1 + 14i_2 = 20$$

$$i_1 = -3.2 \text{ A}$$

KCL

$$i_2 = i_1 + 6$$

$$i_2 = 2.8 \text{ A}$$

A **supermesh** results when two meshes have a (dependent or independent) current source in common.


EHB 211E

7

7

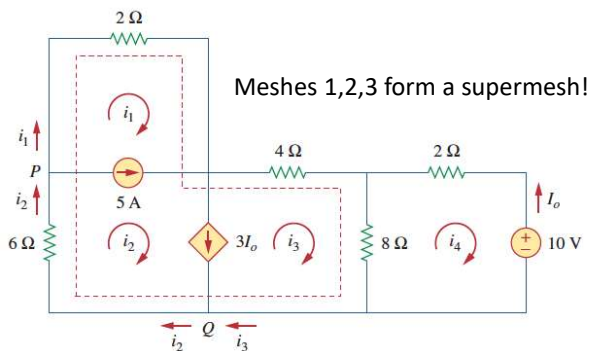Exercise

For the below circuit, find mesh currents



KVL on supermesh

$$2i_1 + 4i_3 + 8(i_3 - i_4) + 6i_2 = 0$$

$$i_1 + 3i_2 + 6i_3 - 4i_4 = 0 \quad (1)$$

KCL at node P,Q

$$i_2 = i_1 + 5 \quad (2) \quad i_2 = i_3 + 3I_o$$

$$I_o = -i_4,$$

$$i_2 = i_3 - 3i_4 \quad (3)$$

KVL on mesh 4

$$2i_4 + 8(i_4 - i_3) + 10 = 0$$

$$5i_4 - 4i_3 = -5 \quad (4)$$

4 equations, 4 unknowns

$$i_1 = -7.5 \text{ A}, \quad i_2 = -2.5 \text{ A}, \quad i_3 = 3.93 \text{ A}, \quad i_4 = 2.143 \text{ A}$$

EHB 211E

8

8

Nodal vs. Mesh Analysis

Circuits containing many series-connected elements -> mesh analysis
 Circuits containing many parallel-connected elements -> nodal analysis

Circuits with fewer nodes than meshes -> nodal analysis
 Circuits with fewer meshes than nodes -> mesh analysis

If one needs to find voltage -> nodal analysis
 If one needs to find branch or mesh currents -> mesh analysis

IT IS BEST TO BE FAMILIAR WITH BOTH METHODS

EHB 211E

9

9

Linearity

1) Homogeneity: If input is multiplied by a constant -> output is multiplied by the same constant:

$$v = iR$$

$$kiR = kv$$

2) Additivity: Sum of inputs is the sum of the responses to each input separately.

$$v_1 = i_1 R$$

$$v_2 = i_2 R$$

$$v = (i_1 + i_2)R = i_1 R + i_2 R = v_1 + v_2$$

A resistor is linear, because the voltage-current relationship satisfies both homogeneity and additivity properties

A linear circuit is one whose output is linearly related to its input


EHB 211E

10

10

Linearity

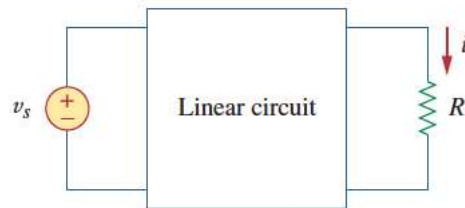Relationship between input voltage and output power is nonlinear



$$\left. \begin{aligned} p_1 &= Ri_1^2 \\ p_2 &= Ri_2^2 \end{aligned} \right\} R(i_1 + i_2)^2 = Ri_1^2 + Ri_2^2 + 2Ri_1i_2 \neq p_1 + p_2$$


EHB 211E

11

11

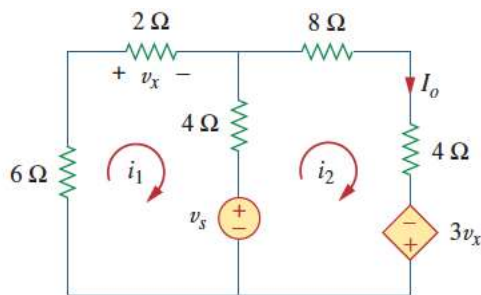Exercise

For the circuit below, find I_o when $v_s = 12\text{V}$ and $v_s = 24\text{V}$



KVL to 2 loops:

$$12i_1 - 4i_2 + v_s = 0 \quad (1)$$

$$-4i_1 + 16i_2 - 3v_x - v_s = 0 \quad v_x = 2i_1$$

$$-10i_1 + 16i_2 - v_s = 0 \quad (2)$$

From (1) and (2), for $v_s = 12\text{V}$ $I_o = i_2 = \frac{12}{76}\text{A}$

for $v_s = 24\text{V}$ $I_o = i_2 = \frac{24}{76}\text{A}$

When source doubles, I_o doubles


EHB 211E

12

12

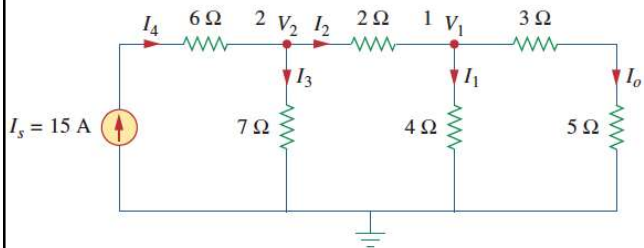Exercise

For the circuit below, assume $I_o = 1A$. Use linearity to find the actual value of I_o .



at node 1

$$V_1 = (3 + 5)I_o = 8 \text{ V}$$

$$I_1 = V_1/4 = 2 \text{ A} \quad \text{Ohm's law}$$

$$I_2 = I_1 + I_o = 3 \text{ A} \quad \text{KCL at node 1}$$

at node 2

$$V_2 = V_1 + 2I_2 = 8 + 6 = 14 \text{ V}$$

$$I_3 = \frac{V_2}{7} = 2 \text{ A} \quad \text{Ohm's law}$$

$$I_4 = I_3 + I_2 = 5 \text{ A} \quad \text{KCL at node 2}$$

$$I_s = 5 \text{ A} \quad \text{Since } I_s \text{ is actually } 15 \text{ A}$$

$$I_o = 3 \text{ A}$$

EHB 211E

13

13

Superposition

Superposition theorem states that voltage across (or current through) an element in a linear circuit is the algebraic sum of the voltage across (current through) that element due to each independent source acting alone.

STEPS:

- 1) Turn off all independent sources except one
 -> replace voltage source with 0V (short circuit)
 -> replace current source with 0A (open circuit)
 Find the output (voltage or current) due to that active source
- 2) Repeat step 1 for all independent sources
- 3) Find the total contribution by adding algebraically all the contributions due to independent sources

Disadvantage -> It involves more work. If the circuit has 3 independent, you'll have to analyze three simpler circuits

Advantage -> Superposition reduces a complex circuit to simpler circuits

- Superposition is based on linearity -> Can not be used for power calculation


EHB 211E

14

14

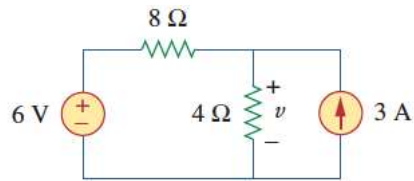
Exercise

Use the superposition theorem to find v in the circuit below




$$v = v_1 + v_2$$

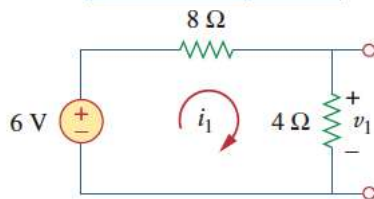v_1 and v_2 are the contributions due to the 6V voltage source and 3A current source



$$12i_1 - 6 = 0 \Rightarrow i_1 = 0.5 \text{ A}$$

$$v_1 = 4i_1 = 2 \text{ V}$$

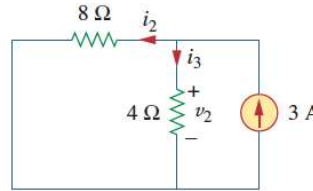

$$i_3 = \frac{8}{4 + 8}(3) = 2 \text{ A} \quad v_2 = 4i_3 = 8 \text{ V}$$

$$v = v_1 + v_2 = 2 + 8 = 10 \text{ V}$$


EHB 211C

15

15

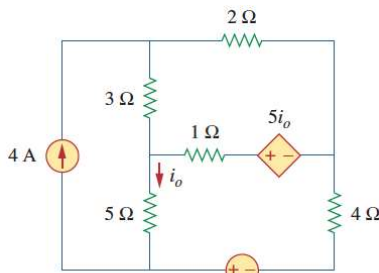
Exercise

Use the superposition theorem to find i_o in the circuit below



$$i_o = i'_o + i''_o$$

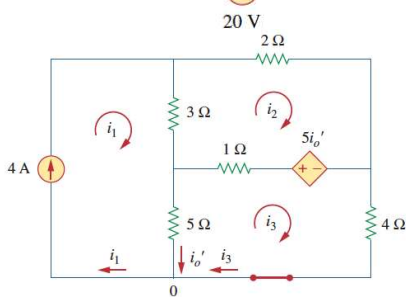i'_o and i''_o are the contributions due to the 4A current source and 20V voltage source



$$i_1 = 4 \text{ A} \quad \text{Loop 1}$$

$$-3i_1 + 6i_2 - 1i_3 - 5i'_o = 0 \quad \text{Loop 2}$$

$$-5i_1 - 1i_2 + 10i_3 + 5i'_o = 0 \quad \text{Loop 3}$$

$$i_3 = i_1 - i'_o = 4 - i'_o \quad \text{KCL at node 0}$$

3 loop equations, 3 unknowns

$$(\text{after inserting KCL eq. into loop 2\&3 equations}) \quad i'_o = \frac{52}{17} \text{ A}$$


EHB 211E

16

16

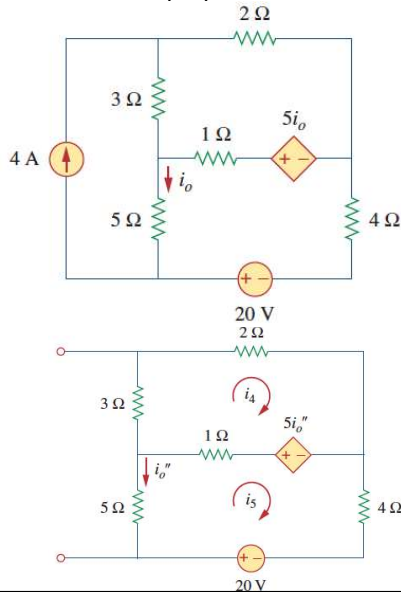Exercise (continued...)

Use the superposition theorem to find i_o in the circuit below



$$i_o = i_o' + i_o''$$

i_o' and i_o'' are the contributions due to the 4A current source and 20V voltage source

$$6i_4 - i_5 - 5i_o'' = 0 \quad \text{Loop 4}$$

$$-i_4 + 10i_5 - 20 + 5i_o'' = 0 \quad \text{Loop 5}$$

$$i_5 = -i_o''$$

2 loop equations, 2 unknowns

(after inserting last eq. into loop 4&5 equations)

$$i_o = i_o' + i_o'' \quad i_o' = \frac{52}{17} \text{ A} \quad i_o'' = -\frac{60}{17} \text{ A}$$

EHB


$$i_o = -\frac{8}{17} = -0.4706 \text{ A}$$

17

17

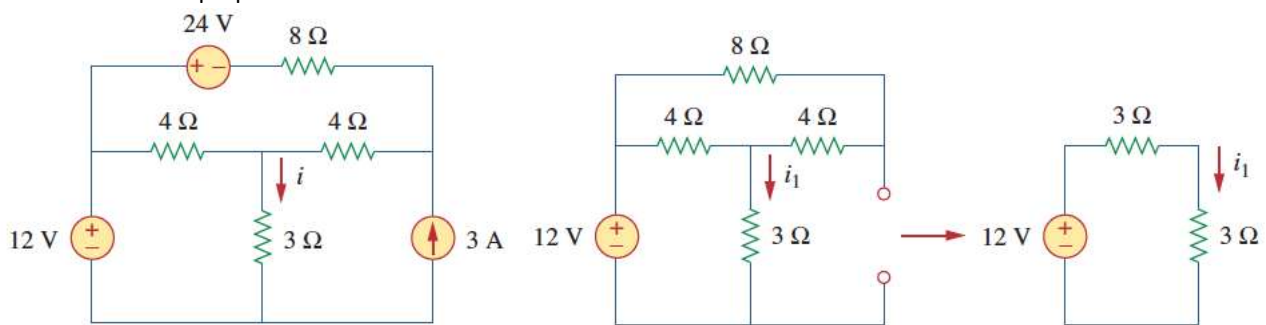Exercise

Use the superposition theorem to find i in the circuit below



$$i = i_1 + i_2 + i_3$$

$$i_1 = \frac{12}{6} = 2 \text{ A}$$

EHB 211E

18

18

Exercise (continued...)

Use the superposition theorem to find i in the circuit below

$$16i_a - 4i_b + 24 = 0 \quad \Rightarrow \quad 4i_a - i_b = -6$$

$$7i_b - 4i_a = 0 \quad \Rightarrow \quad i_a = \frac{7}{4}i_b$$

$$i_2 = i_b = -1$$

$$3 = \frac{v_2}{8} + \frac{v_2 - v_1}{4}$$

$$\frac{v_2 - v_1}{4} = \frac{v_1}{4} + \frac{v_1}{3}$$

$$i_3 = \frac{v_1}{3} = 1 \text{ A}$$


$i = i_1 + i_2 + i_3 = 2 - 1 + 1 = 2 \text{ A}$

EHB 211E

19

Source Transformation

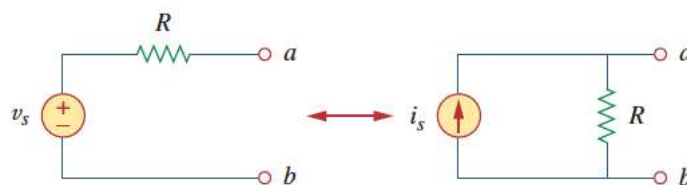Source transformation is a technique to simplify circuits:



Source transformation is the process of replacing a voltage source (dependent or independent) with a resistor, by a current source (dependent or independent) with the same resistor in parallel.

Two circuits are equivalent and replaceable, provided that they have the same voltage-current relationship at terminals a-b.

-> If the sources are turned off, the equivalent resistance at terminal a-b is R for both circuits

-> Short circuit current at terminal a-b is:

$i_{sc} = v_s/R$ for the circuit on the left and $i_{sc} = i_s$ for the circuit on the right. Source transformation requires:

$$v_s = i_s R \quad \text{or} \quad i_s = \frac{v_s}{R}$$


... 3 211E

20

20

Exercise

Use source transformation to find v_o

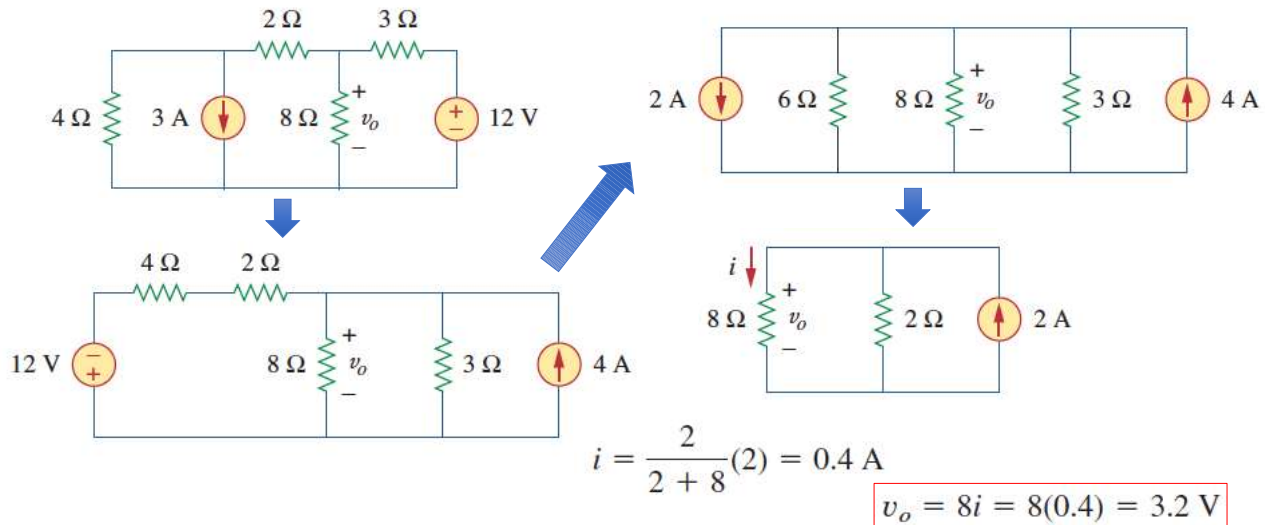


EHB 211E

21

21

Exercise

Use source transformation to find v_x

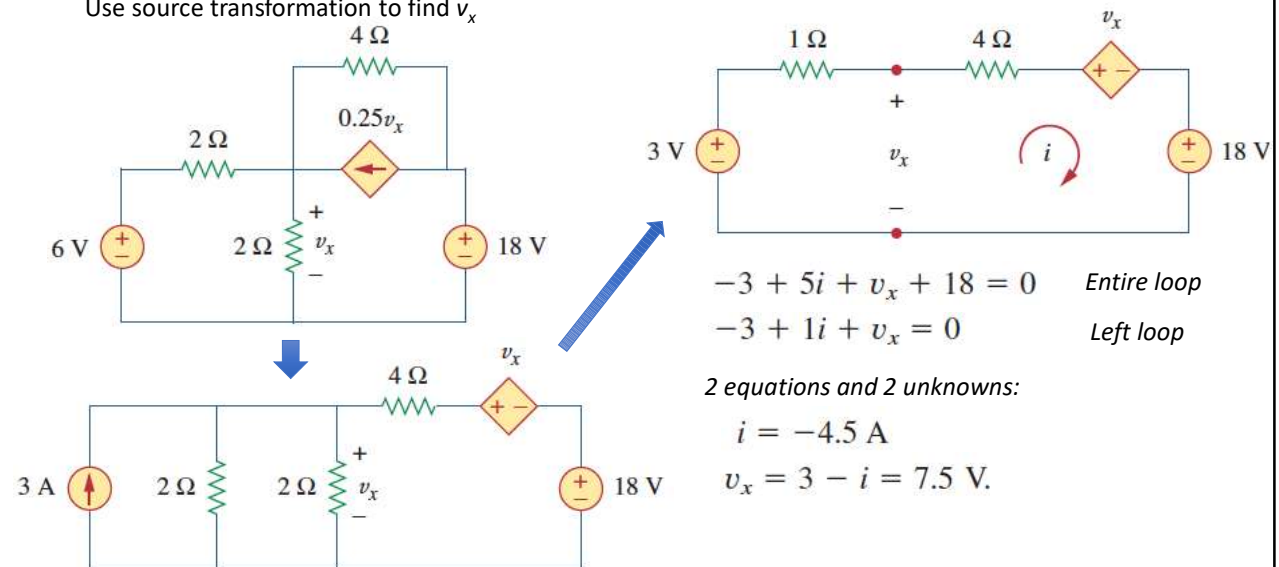

EHB 211E

22

22