

EHB 211E: Basics of Electrical Circuits


Asst. Prof. Ahmet Can Erten
(aerten@itu.edu.tr)

1

Network Topology: Nodes, Branches, and Loops

Elements of an electrical circuit can be interconnected in several ways. Some terminology is given below:

- A **branch** represents a single (*two-terminal*) element such as a voltage source or a resistor
below circuit has 5 branches.
- A **node** is the point of connection between two or more branches
(if a short circuit, a connection wire, connects two nodes, the two nodes constitute a single node)
below circuit has 3 nodes (a, b, c).
- A **loop** is any closed path in a circuit.
(starting from a node, and returning to the same node without passing through any node more than once). A loop is *independent*, if it contains at least one branch which is not part of any other independent loop. Independent loops ($l=3$ for the circuit below) result in independent set of equations.

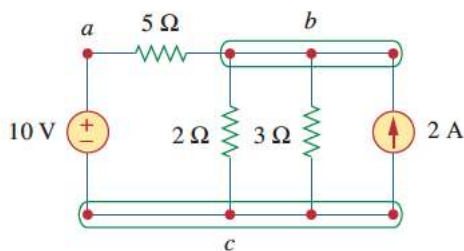

A network of b branches, n nodes, and l independent loops will satisfy the fundamental theorem of network topology:

$$b = l + n - 1$$

EHB 211E

2



2

Kirchhoff's Laws - KCL

Kirchhoff's Current Law (KCL) states that algebraic sum of currents entering a node (or closed boundary) is zero.

$$\sum_{n=1}^N i_n = 0$$

Where, N is the number of branches entering the node, i_n is the n_{th} current entering the node

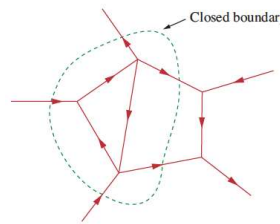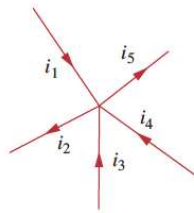

EHB 211E

3

3

Kirchhoff's Laws - KCL


The algebraic sum of currents at a node:

$$i_T(t) = i_1(t) + i_2(t) + i_3(t) + \dots$$

integrate

$$q_T(t) = q_1(t) + q_2(t) + q_3(t) + \dots$$

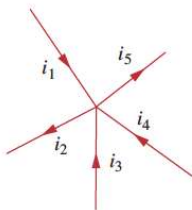Conservation of charge: Sum of electrical charge at a node must not change $\rightarrow i_T(t) = 0$



$$i_1 + (-i_2) + i_3 + i_4 + (-i_5) = 0$$

$$i_1 + i_3 + i_4 = i_2 + i_5$$


KCL (alternative): The sum of currents entering a node is equal to the sum of currents leaving a node.

EHB 211E

4

4


Kirchhoff's Laws - KCL

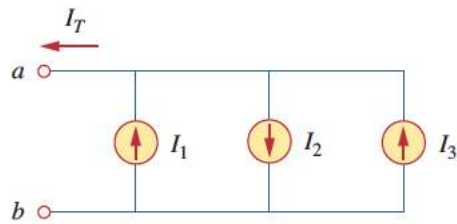

$$I_T + I_2 = I_1 + I_3$$

$$I_T = I_1 - I_2 + I_3$$

Equivalent circuit

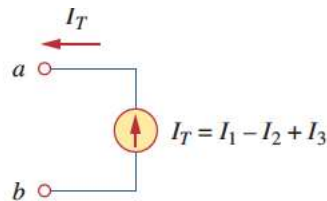

EHB 211E

5


5

Kirchhoff's Laws - KVL

Kirchhoff's Voltage Law (KVL) states that algebraic sum of all voltages around a closed path (loop) is zero.

$$\sum_{m=1}^M v_m = 0$$

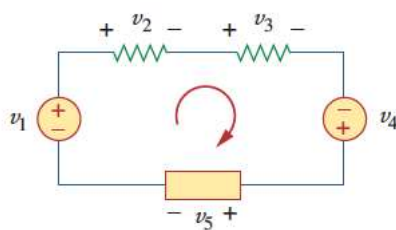Where, M is the number of voltages in the loop, and v_m is the m_{th} voltage.



$$-v_1 + v_2 + v_3 - v_4 + v_5 = 0$$

$$v_2 + v_3 + v_5 = v_1 + v_4$$


Sum of voltage drops = sum of voltage rises.

EHB 211E

6

6

Kirchhoff's Laws - KVL

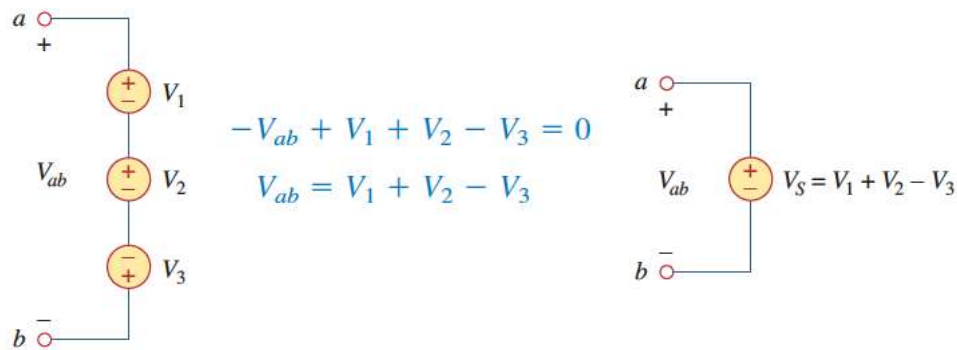


EHB 211E

7

7

Exercise

For the circuit below, Find v_1 and v_2

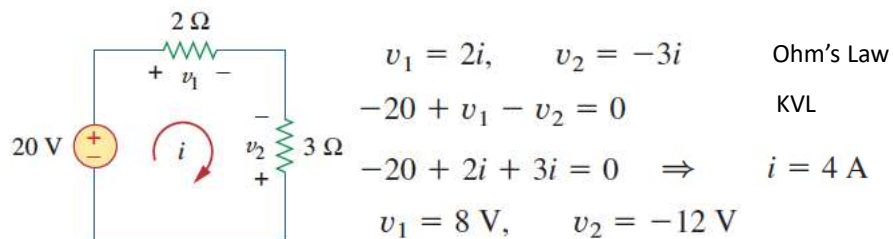


EHB 211E

8

8

Exercise

For the circuit below, Find v_o and i

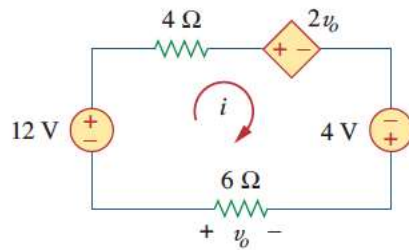

$$-12 + 4i + 2v_o - 4 + 6i = 0 \quad \text{KVL}$$

$$v_o = -6i \quad \text{Ohm's Law}$$

$$-16 + 10i - 12i = 0 \quad \Rightarrow \quad i = -8 \text{ A}$$

$$v_o = 48 \text{ V.}$$


EHB 211E

9

9

Exercise

For the circuit below, Find v_o and i_o

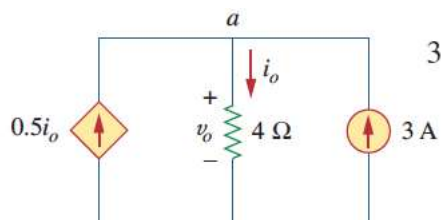

$$3 + 0.5i_o = i_o \quad \Rightarrow \quad i_o = 6 \text{ A} \quad \text{KCL}$$

$$v_o = 4i_o = 24 \text{ V} \quad \text{Ohm's Law}$$


EHB 211E

10

10

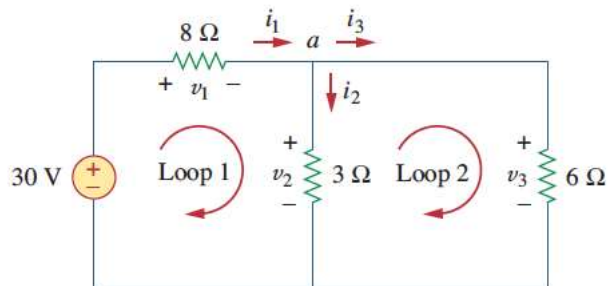Exercise

For the circuit below, Find the voltages and currents



$$v_1 = 8i_1, \quad v_2 = 3i_2, \quad v_3 = 6i_3$$

$$i_1 - i_2 - i_3 = 0 \quad (1)$$

$$-30 + v_1 + v_2 = 0$$

$$-30 + 8i_1 + 3i_2 = 0$$

$$i_1 = \frac{(30 - 3i_2)}{8} \quad (2)$$

$$-v_2 + v_3 = 0 \Rightarrow v_3 = v_2$$

$$6i_3 = 3i_2 \Rightarrow i_3 = \frac{i_2}{2} \quad (3)$$

$$\frac{30 - 3i_2}{8} - i_2 - \frac{i_2}{2} = 0 \quad (1,2,3) \quad i_2 = 2 \text{ A}$$


$$i_1 = 3 \text{ A}, \quad i_3 = 1 \text{ A}, \quad v_1 = 24 \text{ V}, \quad v_2 = 6 \text{ V}, \quad v_3 = 6 \text{ V}$$

EHB 211E

11

11

Series Resistors and Voltage Division

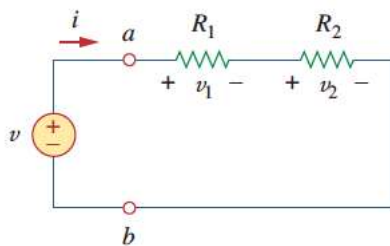

$$v_1 = iR_1, \quad v_2 = iR_2$$

$$v = v_1 + v_2 = i(R_1 + R_2) \quad i = \frac{v}{R_1 + R_2}$$

$$v = iR_{eq}$$

$$R_{eq} = R_1 + R_2$$

VOLTAGE DIVISION

Equivalent resistance of any number of serially connected resistors is the sum of the individual resistances

$$v_1 = \frac{R_1}{R_1 + R_2} v, \quad v_2 = \frac{R_2}{R_1 + R_2} v$$


$$R_{eq} = R_1 + R_2 + \cdots + R_N = \sum_{n=1}^N R_n$$

EHB 211E

12

12

Parallel Resistors and Current Division

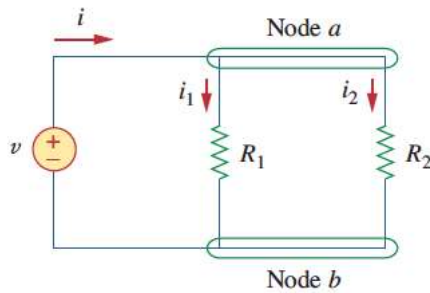

$$v = i_1 R_1 = i_2 R_2$$

$$i_1 = \frac{v}{R_1}, \quad i_2 = \frac{v}{R_2}$$

$$i = i_1 + i_2$$

$$i = \frac{v}{R_1} + \frac{v}{R_2} = v \left(\frac{1}{R_1} + \frac{1}{R_2} \right) = \frac{v}{R_{eq}}$$

$$R_{eq} = \frac{R_1 R_2}{R_1 + R_2}$$

CURRENT DIVISION

Equivalent resistance of two parallel resistors is equal to the product of their resistances divided by their sum

$$i_1 = \frac{R_2 i}{R_1 + R_2}, \quad i_2 = \frac{R_1 i}{R_1 + R_2}$$

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \cdots + \frac{1}{R_N}$$



EHB 211E

13

13

Equivalent Conductance

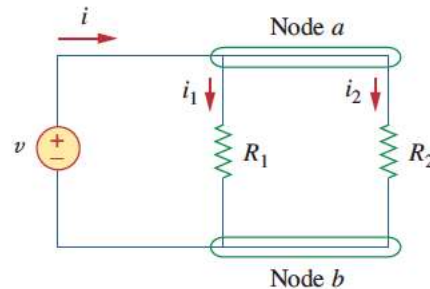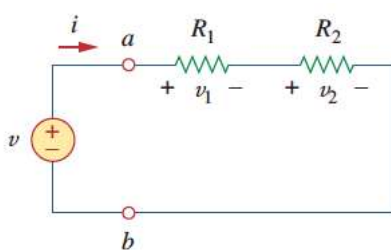equivalent conductance for series / parallel conductance shows opposite behavior to the calculation of equivalent resistance (derive the formulas as an exercise)



$$\frac{1}{G_{eq}} = \frac{1}{G_1} + \frac{1}{G_2} + \frac{1}{G_3} + \cdots + \frac{1}{G_N}$$

$$G_{eq} = G_1 + G_2 + G_3 + \cdots + G_N$$


EHB 211E

14

14

Exercise

Find R_{eq}

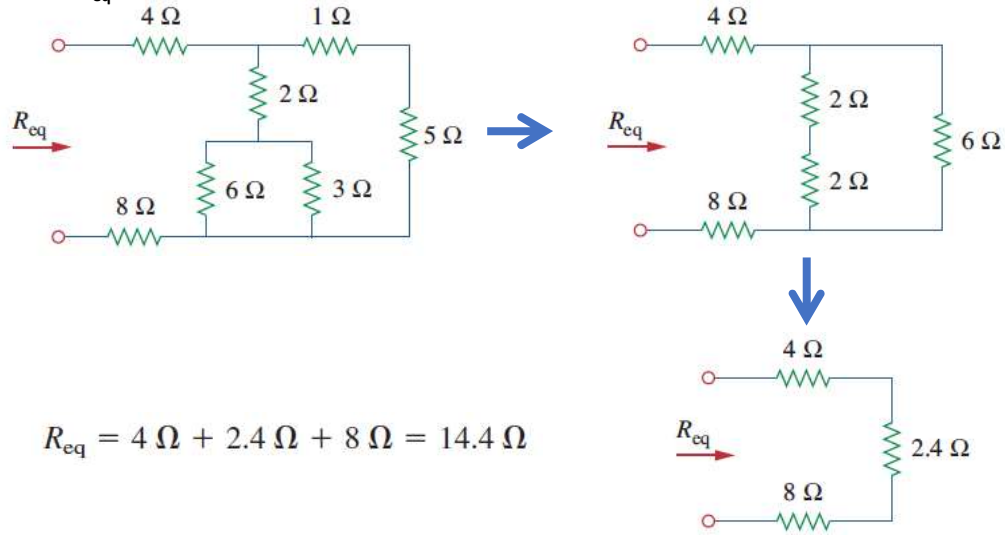


EHB 211E

15

15

Exercise

Find R_{ab}

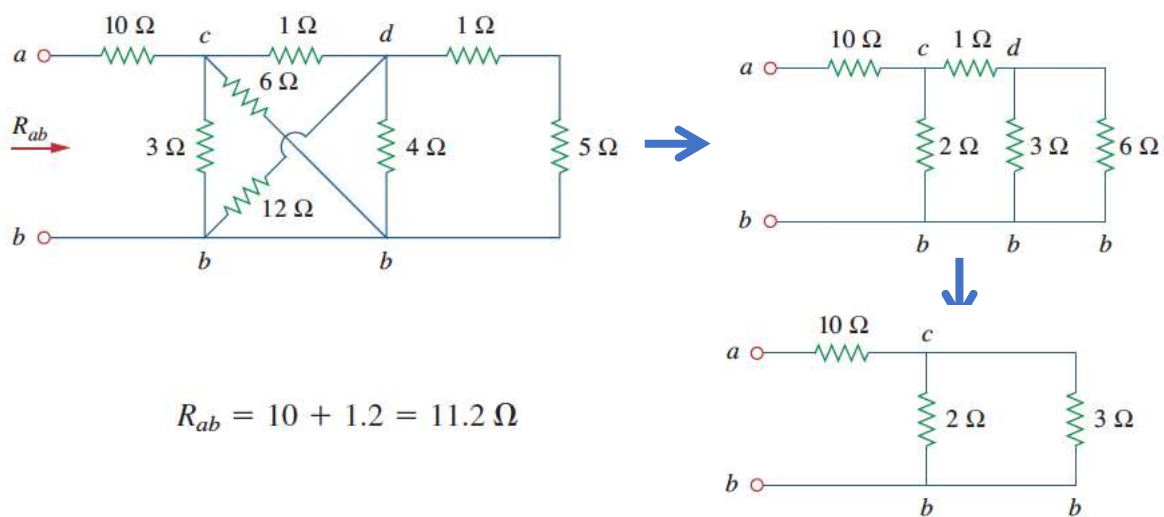


EHB 211E

16

16

Exercise

Find G_{eq}

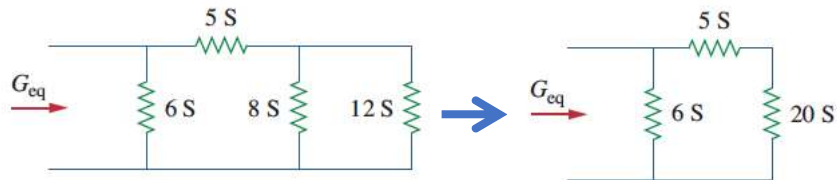

$$G_{eq} = (20 \cdot 5) / (20 + 5) + 6 = 10 \text{ S}$$


EHB 211E

17

17

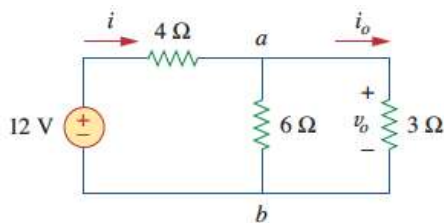
Exercise

Find v_o , i_o . Calculate the power dissipated by the 3Ω resistor.



$$v_o = \frac{2}{2 + 4} (12 \text{ V}) = 4 \text{ V}$$

Voltage division

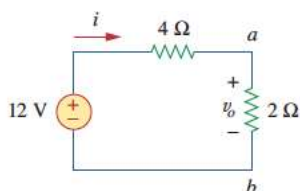

$$v_o = 3i_o = 4 \Rightarrow i_o = \frac{4}{3} \text{ A} \quad \text{Ohm's Law}$$

$$i_o = \frac{6}{6 + 3} i = \frac{2}{3} (2 \text{ A}) = \frac{4}{3} \text{ A} \quad \text{Alternative way of finding } i_o: \text{ current division}$$

$$p_o = v_o i_o = 4 \left(\frac{4}{3} \right) = 5.333 \text{ W}$$


EHB 211E

18

18

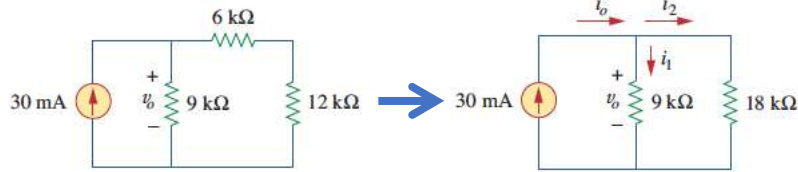Exercise

Find v_o , power supplied by the current source, power absorbed by each resistor



$$i_1 = \frac{18,000}{9,000 + 18,000} (30 \text{ mA}) = 20 \text{ mA}$$

$$i_2 = \frac{9,000}{9,000 + 18,000} (30 \text{ mA}) = 10 \text{ mA}$$

Power supplied by the source:

$$p_o = v_o i_o = 180(30) \text{ mW} = 5.4 \text{ W}$$

$$v_o = 9,000 i_1 = 18,000 i_2 = 180 \text{ V}$$

$$\text{Alternatively: } v_o = 30 \cdot R_{eq} = 180 \text{ V}$$

Power absorbed by the 12-kΩ resistor is

$$p = iv = i_2(i_2 R) = i_2^2 R = (10 \times 10^{-3})^2 (12,000) = 1.2 \text{ W}$$

Power absorbed by the 9-kΩ resistor is

$$p = v_o i_1 = 180(20) \text{ mW} = 3.6 \text{ W}$$

Power absorbed by the 6-kΩ resistor is

$$p = i_2^2 R = (10 \times 10^{-3})^2 (6,000) = 0.6 \text{ W}$$

Tellegen's theorem is satisfied!
Power supplied = total power dissipated

EHB 211E



19

19


Wye-Delta Transformation

Conditions may occur (like below), where resistors are neither in series nor parallel!

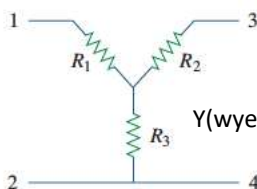
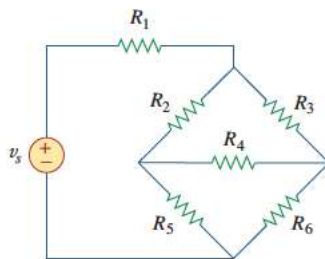
Transforming the circuit, allows finding equivalent resistance.



Y(wye) – T circuits

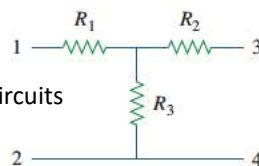

Δ (Delta) – Π (pi) circuits

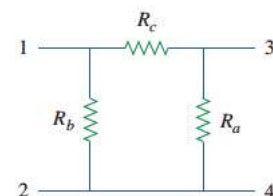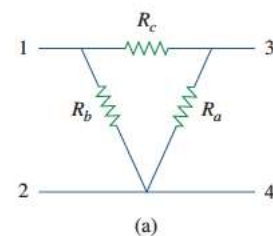


EHB 211E

20

20

Delta-Wye conversion

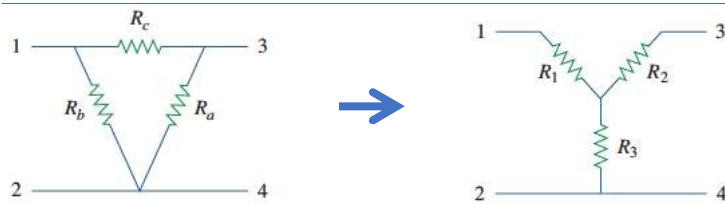

$$R_{12}(Y) = R_1 + R_3 \rightarrow R_{12}(Y) = R_{12}(\Delta) \rightarrow R_{12} = R_1 + R_3 = \frac{R_b(R_a + R_c)}{R_a + R_b + R_c} \quad (1)$$

$$R_{12}(\Delta) = R_b \parallel (R_a + R_c)$$

$$R_{13} = R_1 + R_2 = \frac{R_c(R_a + R_b)}{R_a + R_b + R_c} \quad (2)$$

$$R_1 = \frac{R_b R_c}{R_a + R_b + R_c} \quad R_1 - R_2 = \frac{R_c(R_b - R_a)}{R_a + R_b + R_c} \quad R_{34} = R_2 + R_3 = \frac{R_a(R_b + R_c)}{R_a + R_b + R_c} \quad (3)$$

$$R_2 = \frac{R_c R_a}{R_a + R_b + R_c}$$

$$R_3 = \frac{R_a R_b}{R_a + R_b + R_c}$$

EHB 211E

21

21

Wye-Delta conversion



$$(1) \quad R_1 = \frac{R_b R_c}{R_a + R_b + R_c}$$

$$(2) \quad R_2 = \frac{R_c R_a}{R_a + R_b + R_c}$$

$$(3) \quad R_3 = \frac{R_a R_b}{R_a + R_b + R_c}$$

$$R_1 R_2 + R_2 R_3 + R_3 R_1 = \frac{R_a R_b R_c (R_a + R_b + R_c)}{(R_a + R_b + R_c)^2} = \frac{R_a R_b R_c}{R_a + R_b + R_c}$$

Divide by eq. 1,2,3

$$R_a = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_1}$$

$$R_b = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_2}$$

$$R_c = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_3}$$


EHB 211E

22

22

Exercise

Obtain R_{ab} for below circuit.

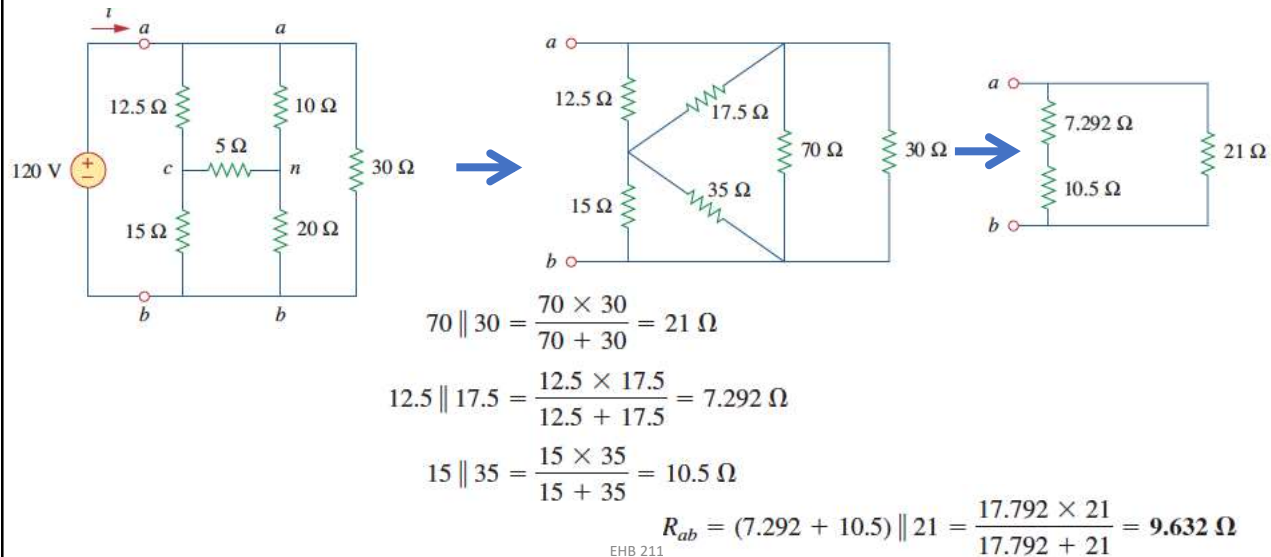

23

Nodal Analysis

Nodal analysis provides a general procedure for analyzing circuits using nodes.

Steps to determine node voltages are:

- 1) Select a node as the reference node. Assign v_1, v_2, \dots, v_{n-1} .
The voltages are referenced with respect to the reference node.
- 2) Apply KCL to each $n-1$ non-reference node.
Use Ohm's law to express branch currents in terms of node voltages
- 3) Solve the resulting simultaneous equations to obtain the unknown node voltages

reference nodes




EHB 211E

24

24

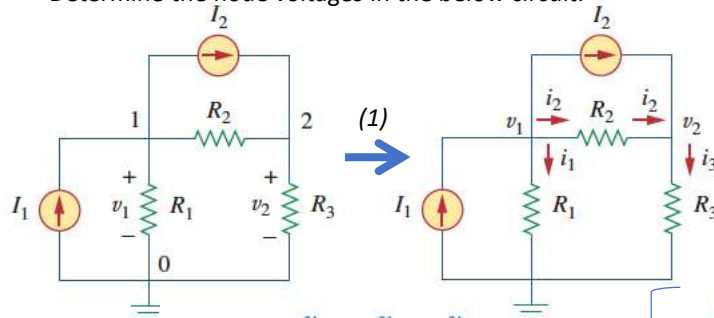Exercise

Determine the node voltages in the below circuit.



$$(2) \quad I_1 = I_2 + i_1 + i_2$$

$$I_2 + i_2 = i_3$$

$$i = \frac{v_{\text{higher}} - v_{\text{lower}}}{R}$$

$$i_1 = \frac{v_1 - 0}{R_1} \quad \text{or} \quad i_1 = G_1 v_1$$

$$i_2 = \frac{v_1 - v_2}{R_2} \quad \text{or} \quad i_2 = G_2(v_1 - v_2)$$

$$i_3 = \frac{v_2 - 0}{R_3} \quad \text{or} \quad i_3 = G_3 v_2$$

$$I_1 = I_2 + \frac{v_1}{R_1} + \frac{v_1 - v_2}{R_2}$$

$$I_2 + \frac{v_1 - v_2}{R_2} = \frac{v_2}{R_3}$$

$$I_1 = I_2 + G_1 v_1 + G_2(v_1 - v_2)$$

$$I_2 + G_2(v_1 - v_2) = G_3 v_2$$


EHB 211E

25

25

Exercise

Determine the node voltages in the below circuit.

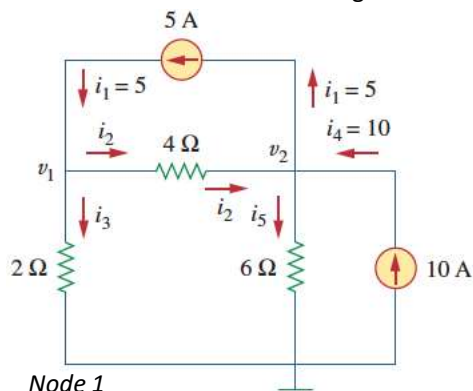

Node 2

$$i_2 + i_4 = i_1 + i_5 \Rightarrow \frac{v_1 - v_2}{4} + 10 = 5 + \frac{v_2 - 0}{6}$$

$$(\times 12) \quad 3v_1 - 3v_2 + 120 = 60 + 2v_2$$

$$-3v_1 + 5v_2 = 60 \quad (2)$$

Using Equations 1 & 2

$$4v_2 = 80 \Rightarrow v_2 = 20 \text{ V}$$

$$i_1 = i_2 + i_3 \Rightarrow 5 = \frac{v_1 - v_2}{4} + \frac{v_1 - 0}{2} \quad \downarrow \quad 3v_1 - 20 = 20 \Rightarrow v_1 = \frac{40}{3} = 13.333 \text{ V}$$

$$20 = v_1 - v_2 + 2v_1 \quad (\times 4)$$

$$3v_1 - v_2 = 20 \quad (1)$$


EHB 211E

26

26

Exercise

Determine the node voltages in the below circuit.

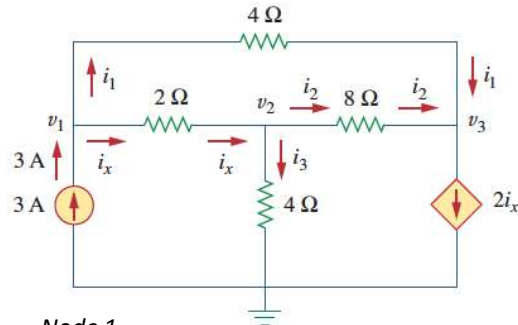

Node 1

$$3 = i_1 + i_x$$

$$3 = \frac{v_1 - v_3}{4} + \frac{v_1 - v_2}{2}$$

$$3v_1 - 2v_2 - v_3 = 12 \quad (\times 4)$$

Node 2

$$i_x = i_2 + i_3 \Rightarrow \frac{v_1 - v_2}{2} = \frac{v_2 - v_3}{8} + \frac{v_2 - 0}{4}$$

$$-4v_1 + 7v_2 - v_3 = 0 \quad (\times 8)$$

Node 3

$$i_1 + i_2 = 2i_x \Rightarrow \frac{v_1 - v_3}{4} + \frac{v_2 - v_3}{8} = \frac{2(v_1 - v_2)}{2}$$

$$2v_1 - 3v_2 + v_3 = 0$$

3 equations, 3 unknowns

$$v_1 = 4.8 \text{ V}, \quad v_2 = 2.4 \text{ V}, \quad v_3 = -2.4 \text{ V}$$

EHB 211E

27


27

Nodal Analysis with Voltage Sources

CASE 1:

If connected between reference and non-reference node, set the voltage of the non-reference node equal to the voltage of the voltage source

$$v_1 = 10 \text{ V}$$

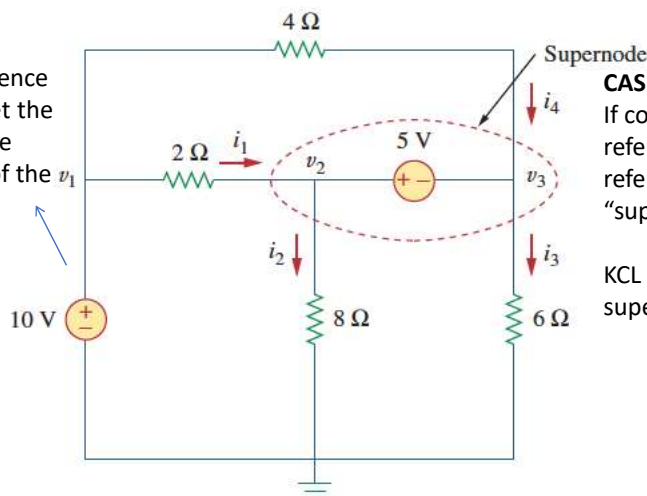

CASE 2:

If connected between two non-reference nodes, the two non-reference nodes form a "supernode".

KCL must be satisfied at the supernode

A **supernode** is formed by enclosing a (dependent or independent) voltage source connected between two nonreference nodes and any elements connected in parallel with it.


EHB 211E

28

28

Nodal Analysis with Voltage Sources

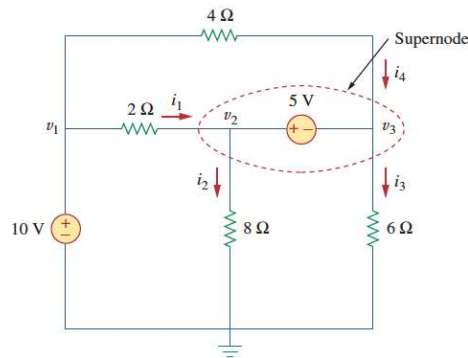Determine the node voltages in the below circuit.



KCL at the supernode


$$i_1 + i_4 = i_2 + i_3$$

$$\frac{v_1 - v_2}{2} + \frac{v_1 - v_3}{4} = \frac{v_2 - 0}{8} + \frac{v_3 - 0}{6}$$

KVL at the supernode

$$-v_2 + 5 + v_3 = 0 \Rightarrow v_2 - v_3 = 5$$

Solution: v_1 is already known
 v_2 and v_3 are dependent
 1 KCL equation, 1 unknown

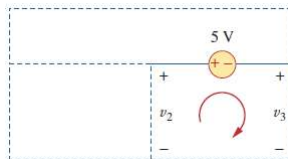


EHB 211E

29

29

Nodal Analysis with Voltage Sources

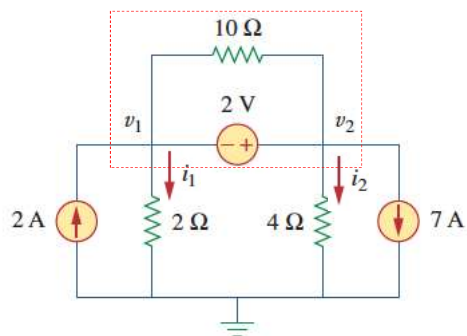Determine the node voltages in the below circuit.



KCL at the supernode

$$2 = i_1 + i_2 + 7$$

$$2 = \frac{v_1 - 0}{2} + \frac{v_2 - 0}{4} + 7 \Rightarrow 8 = 2v_1 + v_2 + 28$$

$$v_2 = -20 - 2v_1 \quad (1)$$

KVL at the supernode

$$-v_1 - 2 + v_2 = 0 \Rightarrow v_2 = v_1 + 2 \quad (2)$$

From 1 & 2:

$$v_1 = -7.333 \text{ V}$$

$$v_2 = v_1 + 2 = -5.333 \text{ V}$$


EHB 211E

30

30

Nodal Analysis with Voltage Sources

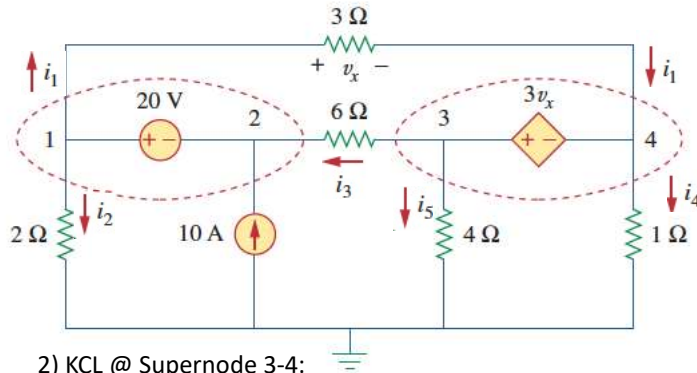Determine the node voltages in the below circuit.



2) KCL @ Supernode 3-4:

$$i_1 = i_3 + i_4 + i_5 \Rightarrow \frac{v_1 - v_4}{3} = \frac{v_3 - v_2}{6} + \frac{v_4}{1} + \frac{v_3}{4}$$

$$4v_1 + 2v_2 - 5v_3 - 16v_4 = 0$$

2 supernodes!

1) KCL @ Supernode 1-2:

$$i_3 + 10 = i_1 + i_2$$

$$\frac{v_3 - v_2}{6} + 10 = \frac{v_1 - v_4}{3} + \frac{v_1}{2}$$

$$5v_1 + v_2 - v_3 - 2v_4 = 60 \quad (\text{re-arrange})$$

3) KVL for 3 independent loops

$$v_1 - v_2 = 20$$

$$-v_3 + 3v_x + v_4 = 0$$

$$v_x = v_1 - v_4$$

$$3v_1 - v_3 - 2v_4 = 0$$


EHB 211E

31

31

Nodal Analysis with Voltage Sources

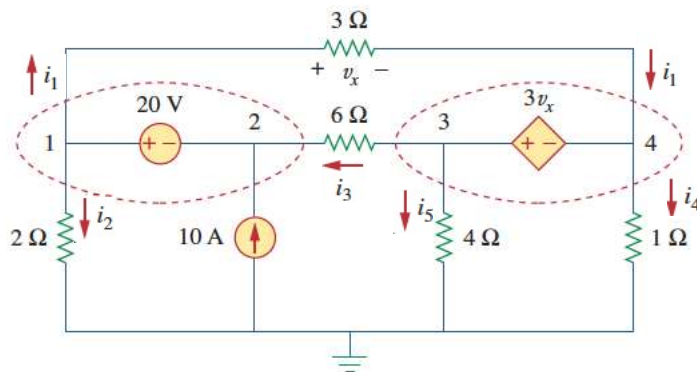Determine the node voltages in the below circuit.



3) KVL for 3 independent loops

$$\text{i) } v_1 - v_2 = 20$$

$$\text{ii) } -v_3 + 3v_x + v_4 = 0$$

$$v_x = v_1 - v_4$$

$$3v_1 - v_3 - 2v_4 = 0$$

$$\text{iii) } v_x - 3v_x + 6i_3 - 20 = 0$$

$$6i_3 = v_3 - v_2$$

$$v_x = v_1 - v_4$$

$$-2v_1 - v_2 + v_3 + 2v_4 = 20$$

4 unknowns, 5 equations (2 equations from KCL, 3 from KVL)
1 equation is redundant / dependent

EHB 211E

32

32