

# EHB 211E: Basics of Electrical Circuits

## *First Order Circuits*

Asst. Prof. Ahmet Can Erten  
(aerten@itu.edu.tr)

1

## Motivation

- We have considered three passive elements: resistors, capacitors, and inductors.
- We will consider circuits that contains various combinations of two or three passive elements:
- In this lecture, we will consider RC & RL circuits (1<sup>st</sup> order circuits)
- RC & RL circuits produce differential equations of the first order  
*A first order circuit is characterized by a first-order differential equation*
- There are two ways to excite the circuits:
  - Initial conditions of the storage elements (*source-free circuits*)  
no independent sources, there may be dependent sources
  - Excitation by independent sources.

EHB 211E

2

2

## The Source-Free RC Circuit

Consider a series combination of R & C elements.

The capacitor is initially charged.

$$v(0) = V_0 \quad w(0) = \frac{1}{2}CV_0^2$$


$$i_C + i_R = 0$$

$$C \frac{dv}{dt} + \frac{v}{R} = 0 \quad \frac{dv}{dt} + \frac{v}{RC} = 0 \quad (\text{First-order differential equation})$$

$$\frac{dv}{v} = -\frac{1}{RC} dt$$

$$\ln v = -\frac{t}{RC} + \ln A \quad A \text{ is the integration constant} \quad v(0) = A = V_0.$$

$$\ln \frac{v}{A} = -\frac{t}{RC} \quad v(t) = Ae^{-t/RC} \quad v(t) = V_0 e^{-t/RC}$$

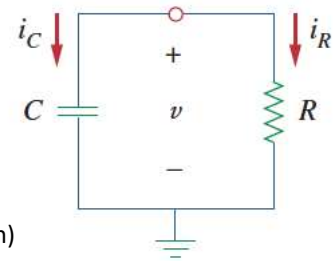

EHB 211E


3

3
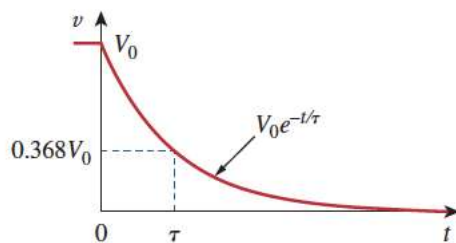
## The Source-Free RC Circuit

$$v(t) = V_0 e^{-t/RC}$$

Voltage response of the RC circuit is an exponential decay of the initial voltage. The response is due to initial energy stored -> **Natural response**




$$\text{At } t = 0, v = v(0) = V_0$$

The time constant ( $\tau$ ) is the time required for the response to decay to a factor of  $1/e$  (36.8%) of its initial value.

$$V_0 e^{-\tau/RC} = V_0 e^{-1} = 0.368V_0$$

$$\tau = RC$$

$$v(t) = V_0 e^{-t/\tau}$$

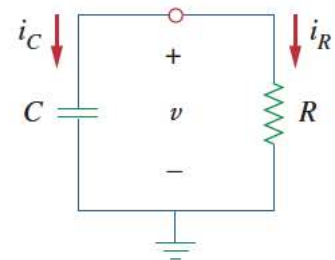

EHB 211E

4


4

## The Source-Free RC Circuit

$$v(t) = V_0 e^{-t/RC}$$


$$v(t) = V_0 e^{-t/\tau}$$

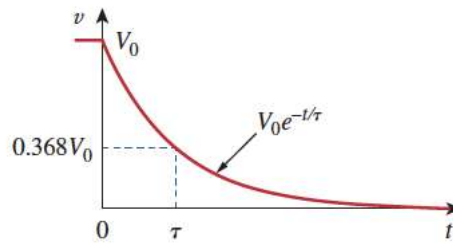- Capacitor is fully discharged after 5 time constants (less than 1% remaining)
- Smaller the time constant, more rapidly the voltage decreases (faster the response)
- A circuit with small time constant reaches steady (final) state quickly.



Values of  $v(t)/V_0 = e^{-t/\tau}$ .

$t$	$v(t)/V_0$
$\tau$	0.36788
$2\tau$	0.13534
$3\tau$	0.04979
$4\tau$	0.01832
$5\tau$	0.00674

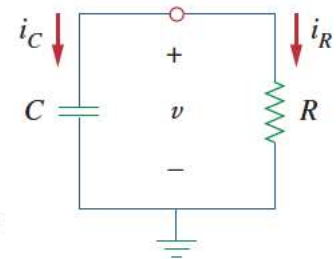

EHB 211E

5



5

## The Source-Free RC Circuit

$$v(t) = V_0 e^{-t/\tau}$$

$$i_R(t) = \frac{v(t)}{R} = \frac{V_0}{R} e^{-t/\tau}$$
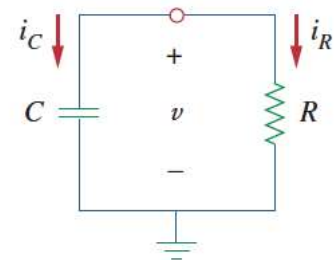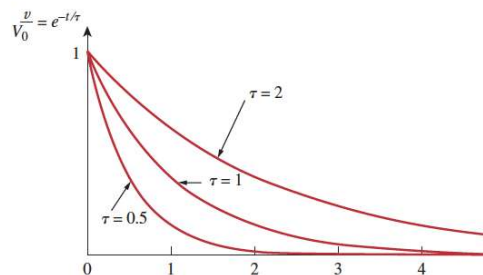
$$p(t) = v i_R = \frac{V_0^2}{R} e^{-2t/\tau}$$



$$w_R(t) = \int_0^t p(\lambda) d\lambda = \int_0^t \frac{V_0^2}{R} e^{-2\lambda/\tau} d\lambda = -\frac{\tau V_0^2}{2R} e^{-2\lambda/\tau} \Big|_0^t = \frac{1}{2} C V_0^2 (1 - e^{-2t/\tau})$$

$$t \rightarrow \infty, w_R(\infty) \rightarrow \frac{1}{2} C V_0^2$$

The energy that was initially stored in the capacitor is eventually dissipated in the resistor.

EHB 211E

6

6

## Exercise

If  $v_C(0) = 15\text{V}$ , find  $v_C$ ,  $v_x$ ,  $i_x$  for  $t > 0$ .

$$R_{\text{eq}} = \frac{20 \times 5}{20 + 5} = 4 \Omega$$



$$\tau = R_{\text{eq}}C = 4(0.1) = 0.4 \text{ s}$$

$$v = v(0)e^{-t/\tau} = 15e^{-t/0.4} \text{ V}, \quad v_C = v = 15e^{-2.5t} \text{ V}$$

Voltage division

$$v_x = \frac{12}{12 + 8}v = 0.6(15e^{-2.5t}) = 9e^{-2.5t} \text{ V}$$

$$i_x = \frac{v_x}{12} = 0.75e^{-2.5t} \text{ A}$$

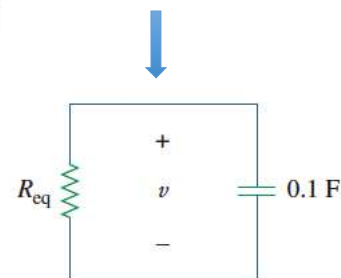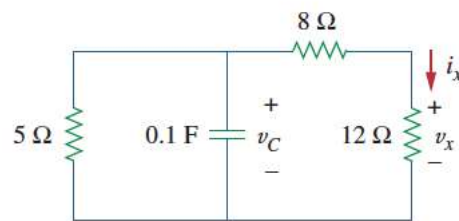

EHB 211E

7

7

## Exercise

The switch has been closed for a long time

The switch is opened at  $t = 0$ . Find  $v(t)$  for  $t > 0$ . Calculate the initial energy stored in the capacitor.

Capacitor is open circuit for  $t < 0$

$$v_C(t) = \frac{9}{9 + 3}(20) = 15 \text{ V}, \quad t < 0$$

Voltage across capacitor can not change instantaneously:

$$v_C(0) = V_0 = 15 \text{ V}$$




$t > 0$

$$R_{\text{eq}} = 1 + 9 = 10 \Omega$$

$$\tau = R_{\text{eq}}C = 10 \times 20 \times 10^{-3} = 0.2 \text{ s}$$

$$v(t) = v_C(0)e^{-t/\tau} = 15e^{-t/0.2} \text{ V} \quad v(t) = 15e^{-5t} \text{ V}$$
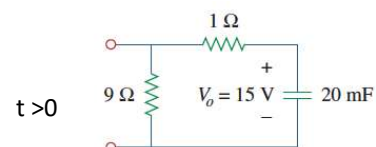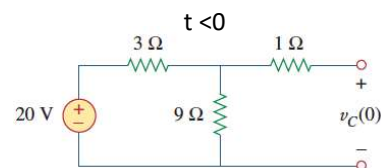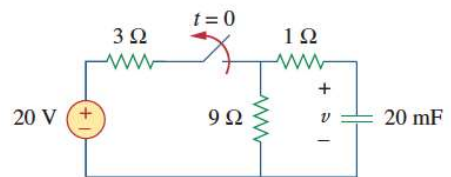
$$w_C(0) = \frac{1}{2}Cv_C^2(0) = \frac{1}{2} \times 20 \times 10^{-3} \times 15^2 = 2.25 \text{ J}$$



8

## The Source-Free RL Circuit

Consider a series combination of R & L elements.

Now, initial inductor current is the response to the circuit

$$i(0) = I_0$$


$$w(0) = \frac{1}{2} L I_0^2$$

$$v_L + v_R = 0$$

$$L \frac{di}{dt} + Ri = 0 \rightarrow \frac{di}{dt} + \frac{R}{L} i = 0 \rightarrow \int_{I_0}^{i(t)} \frac{di}{i} = - \int_0^t \frac{R}{L} dt$$

$$\ln i \Big|_{I_0}^{i(t)} = - \frac{Rt}{L} \Big|_0^t \Rightarrow \ln i(t) - \ln I_0 = - \frac{Rt}{L} + 0 \rightarrow \ln \frac{i(t)}{I_0} = - \frac{Rt}{L}$$

$$i(t) = I_0 e^{-Rt/L}$$

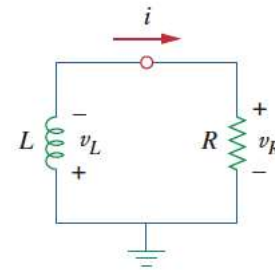

EHB 211E

9



9

## The Source-Free RL Circuit

$$i(t) = I_0 e^{-Rt/L}$$

$$\tau = \frac{L}{R}$$

$$i(t) = I_0 e^{-t/\tau}$$

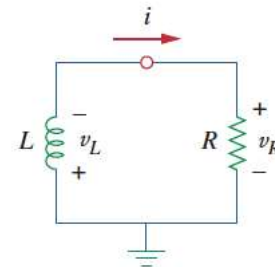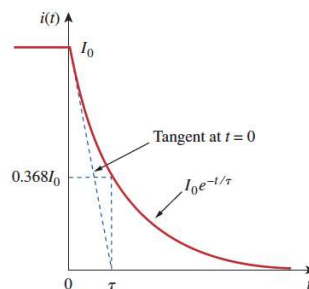

The energy that was initially stored in the inductor is eventually dissipated in the resistor.  $t \rightarrow \infty, w_R(\infty) \rightarrow \frac{1}{2} L I_0^2$

$$v_R(t) = iR = I_0 R e^{-t/\tau}$$

$$p = v_R i = I_0^2 R e^{-2t/\tau} \quad \tau = \frac{L}{R}$$

$$w_R(t) = \int_0^t p(\lambda) d\lambda = \int_0^t I_0^2 R e^{-2\lambda/\tau} d\lambda = -\frac{\tau}{2} I_0^2 R e^{-2\lambda/\tau} \Big|_0^t, \quad w_R(t) = \frac{1}{2} L I_0^2 (1 - e^{-2t/\tau})$$

EHB 211E

10

10

## Exercise

Assuming that  $i(0) = 10\text{ A}$ , calculate  $i(t)$  and  $i_x(t)$ .

**Method 1:** Find Equivalent (Thevenin) resistance

$$2(i_1 - i_2) + 1 = 0 \Rightarrow i_1 - i_2 = -\frac{1}{2}$$

$$6i_2 - 2i_1 - 3i_1 = 0 \Rightarrow i_2 = \frac{5}{6}i_1$$


$$i_1 = -3\text{ A}, \quad i_o = -i_1 = 3\text{ A}$$

$$R_{\text{eq}} = R_{\text{Th}} = \frac{v_o}{i_o} = \frac{1}{3}\Omega$$

$$\tau = \frac{L}{R_{\text{eq}}} = \frac{\frac{1}{2}}{\frac{1}{3}} = \frac{3}{2}\text{ s}$$

$$i(t) = i(0)e^{-t/\tau} = 10e^{-(2/3)t}\text{ A}, \quad t > 0$$

EHB 211E

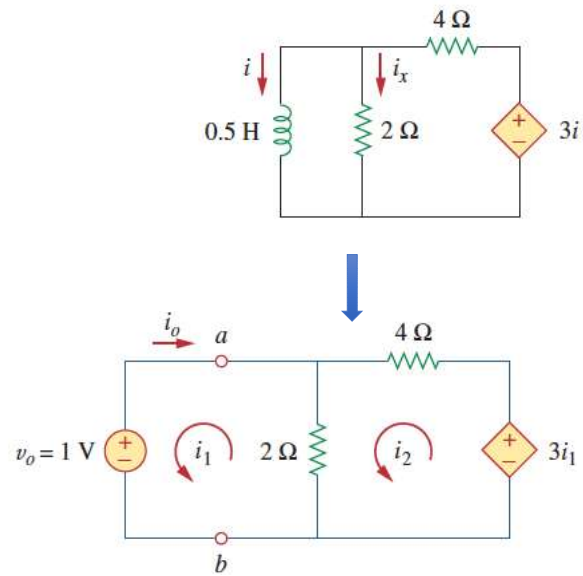

11

11

## Exercise

Assuming that  $i(0) = 10\text{ A}$ , calculate  $i(t)$  and  $i_x(t)$ .

**Method 2:** Directly apply KVL

$$\frac{1}{2} \frac{di_1}{dt} + 2(i_1 - i_2) = 0 \quad 6i_2 - 2i_1 - 3i_1 = 0$$

$$\frac{di_1}{i_1} = -\frac{2}{3}dt$$


$$\ln i \Big|_{i(0)}^{i(t)} = -\frac{2}{3}t \Big|_0^t \quad \ln \frac{i(t)}{i(0)} = -\frac{2}{3}t$$

$$i(t) = i(0)e^{-(2/3)t} = 10e^{-(2/3)t}\text{ A}, \quad t > 0$$

$$v = L \frac{di}{dt} = 0.5(10) \left( -\frac{2}{3} \right) e^{-(2/3)t} = -\frac{10}{3} e^{-(2/3)t}\text{ V}$$

$$i_x(t) = \frac{v}{2} = -1.6667e^{-(2/3)t}\text{ A}, \quad t > 0$$

EHB 211E

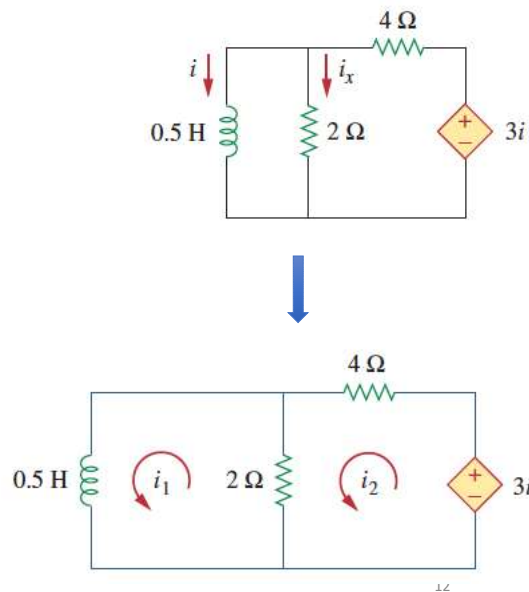

12

12

## Exercise

The switch has been closed for a long time. At  $t = 0$ , the switch opens. Calculate  $i(t)$ .

For  $t < 0$ , the inductor acts as a short circuit

$$\frac{4 \times 12}{4 + 12} = 3 \Omega \quad i_1 = \frac{40}{2 + 3} = 8 \text{ A}$$

$$i(t) = \frac{12}{12 + 4} i_1 = 6 \text{ A}, \quad t < 0$$


Current through an inductor cannot change instantaneously

$$i(0) = i(0^-) = 6 \text{ A}$$

$$R_{eq} = (12 + 4) \parallel 16 = 8 \Omega$$

$$\tau = \frac{L}{R_{eq}} = \frac{2}{8} = \frac{1}{4} \text{ s}$$

$$i(t) = i(0)e^{-t/\tau} = 6e^{-4t} \text{ A}$$

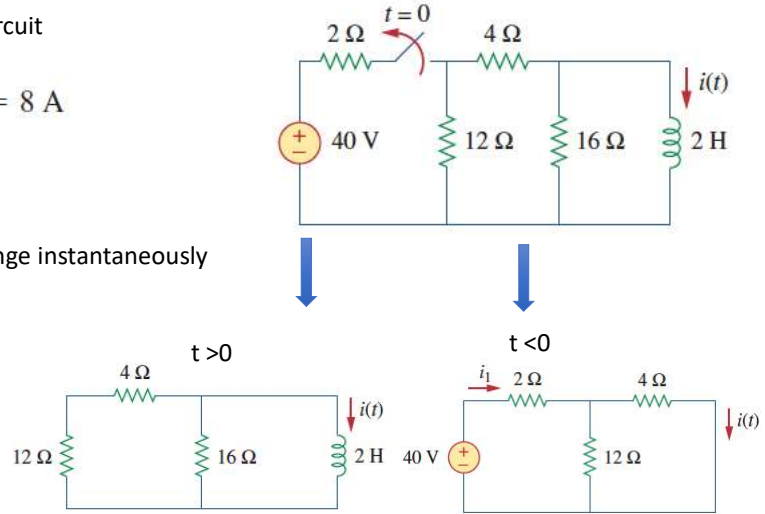

EHB 211E

13

13

## Exercise

The switch has been open for a long time. At  $t = 0$ , the switch closes. Calculate  $i_o(t)$ ,  $v_o(t)$ , and  $i(t)$

$$i(t) = \frac{10}{2 + 3} = 2 \text{ A}, \quad t < 0 \quad i(0) = 2$$

$$v_o(t) = 3i(t) = 6 \text{ V}, \quad t < 0$$


$t > 0$

$$R_{Th} = 3 \parallel 6 = 2 \Omega \quad \tau = \frac{L}{R_{Th}} = 1 \text{ s}$$

$$i(t) = i(0)e^{-t/\tau} = 2e^{-t} \text{ A}, \quad t > 0$$

$$v_o(t) = -v_L = -L \frac{di}{dt} = -2(-2e^{-t}) = 4e^{-t} \text{ V}$$

$$i_o(t) = \frac{v_L}{6} = -\frac{2}{3}e^{-t} \text{ A}, \quad t > 0$$

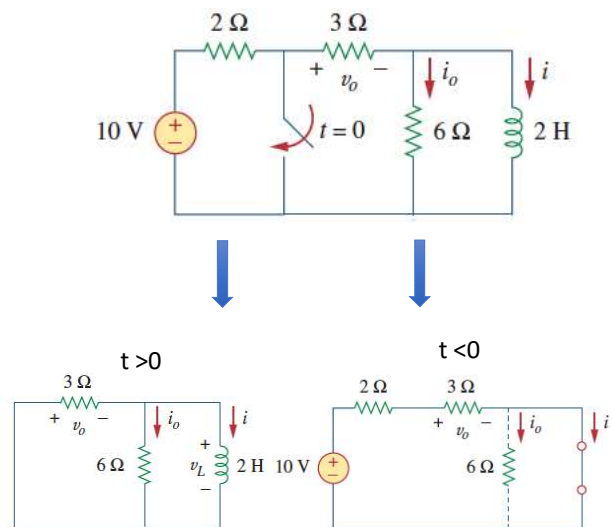

EHB 211E

14

14



## Exercise (continued...)

The switch has been open for a long time. At  $t = 0$ , the switch closes. Calculate  $i_o(t)$ ,  $v_o(t)$ , and  $i(t)$

$$i_o(t) = \begin{cases} 0 \text{ A}, & t < 0 \\ -\frac{2}{3}e^{-t} \text{ A}, & t > 0 \end{cases} \quad v_o(t) = \begin{cases} 6 \text{ V}, & t < 0 \\ 4e^{-t} \text{ V}, & t > 0 \end{cases}$$

All current flows through the inductor, not the resistor
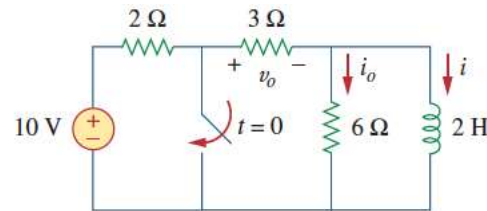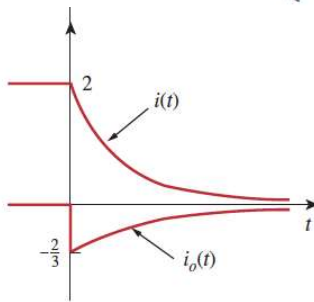
$$i(t) = \begin{cases} 2 \text{ A}, & t < 0 \\ 2e^{-t} \text{ A}, & t \geq 0 \end{cases}$$



Inductor current is continuous while the resistor current makes a jump !

Time constant is the same regardless of what output is taken!

EHB 211E


15

15

## Singularity (switching) Functions

- Singularity functions serve as good approximations to the switching signals that arise in circuits.
- They are helpful in the compact description of step responses of RC and RL circuits.
- Singularity functions are either discontinuous or have discontinuous derivatives.

### Unit step function

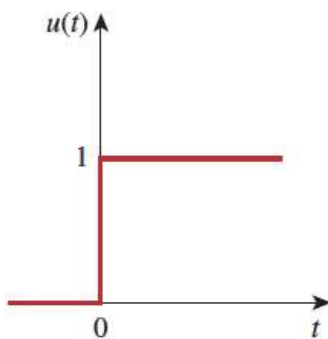

$$u(t) = \begin{cases} 0, & t < 0 \\ 1, & t > 0 \end{cases}$$

$u(t)$  is undefined for  $t = 0$


EHB 211E

16


16



## Unit Step Function

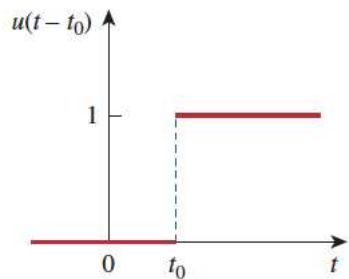
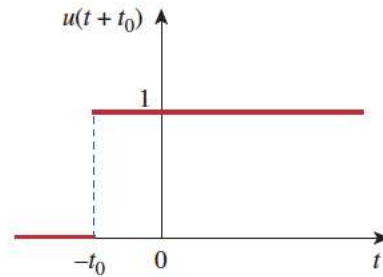
$$u(t - t_0) = \begin{cases} 0, & t < t_0 \\ 1, & t > t_0 \end{cases}$$



$$u(t + t_0) = \begin{cases} 0, & t < -t_0 \\ 1, & t > -t_0 \end{cases}$$

$$v(t) = \begin{cases} 0, & t < t_0 \\ V_0, & t > t_0 \end{cases}$$



$$v(t) = V_0 u(t - t_0)$$

EHB 211E

17


17

## Unit Step Function



$$v(t) = \begin{cases} 0, & t < t_0 \\ V_0, & t > t_0 \end{cases}$$




$$v(t) = V_0 u(t - t_0)$$

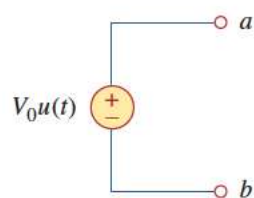

=

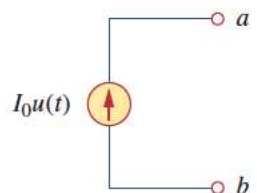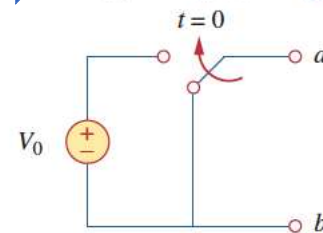

=

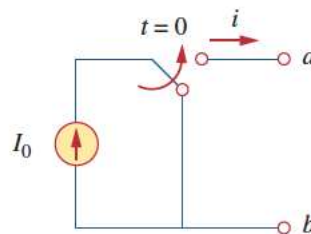


EHB 211E

18

18
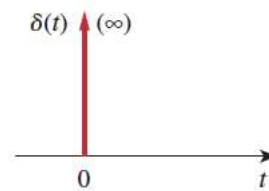
## Unit Impulse Function


$$\delta(t) = \frac{d}{dt}u(t) = \begin{cases} 0, & t < 0 \\ \text{Undefined}, & t = 0 \\ 0, & t > 0 \end{cases}$$



Unit impulse function may be regarded as an applied shock signal.  
It may be visualized as a very short duration of pulse.

$$\int_{0^-}^{0^+} \delta(t) dt = 1$$

Strength of the impulse function

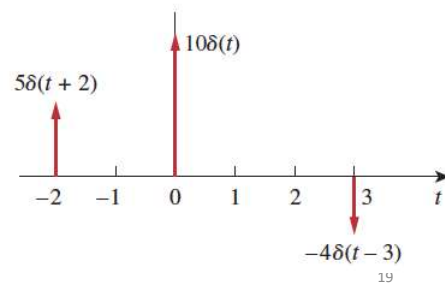

EHB 211E


19

19

## Unit Ramp Function

$$r(t) = \int_{-\infty}^t u(\lambda) d\lambda = tu(t)$$

$$r(t) = \begin{cases} 0, & t \leq 0 \\ t, & t \geq 0 \end{cases}$$

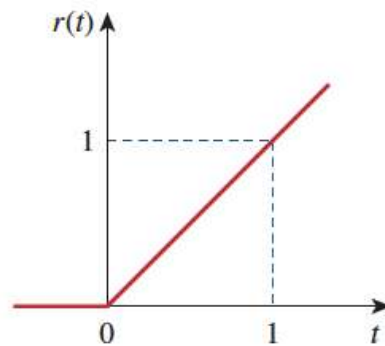

EHB 211E

20

20

## Step Response of an RC Circuit

When the DC source of an RC circuit is suddenly applied, the voltage or current can be modeled as a step function, known as the step response.

Initial voltage on capacitor

$$v(0^-) = v(0^+) = V_0$$

$$C \frac{dv}{dt} + \frac{v - V_s u(t)}{R} = 0$$

$$\frac{dv}{dt} + \frac{v}{RC} = \frac{V_s}{RC} u(t) \quad \xrightarrow{t > 0} \quad \frac{dv}{dt} + \frac{v}{RC} = \frac{V_s}{RC}$$

$$\frac{dv}{dt} = -\frac{v - V_s}{RC} \quad \xrightarrow{\quad} \quad \frac{dv}{v - V_s} = -\frac{dt}{RC}$$


$$\ln(v - V_s) \Big|_{V_0}^{v(t)} = -\frac{t}{RC} \Big|_0^t \quad \ln \frac{v - V_s}{V_0 - V_s} = -\frac{t}{RC}$$

$$v - V_s = (V_0 - V_s)e^{-t/\tau} \quad v(t) = V_s + (V_0 - V_s)e^{-t/\tau}, \quad t > 0$$

EHB 211E 21

21

## Step Response of an RC Circuit

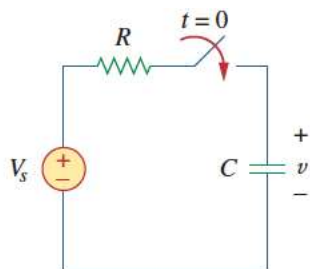


"Complete (total) response"

$$v(t) = \begin{cases} V_0, & t < 0 \\ V_s + (V_0 - V_s)e^{-t/\tau}, & t > 0 \end{cases}$$


If capacitor is initially uncharged:

$$v(t) = \begin{cases} 0, & t < 0 \\ V_s(1 - e^{-t/\tau}), & t > 0 \end{cases} \quad i(t) = C \frac{dv}{dt} = \frac{C}{\tau} V_s e^{-t/\tau}, \quad \tau = RC, \quad t > 0$$

$$v(t) = V_s(1 - e^{-t/\tau})u(t) \quad i(t) = \frac{V_s}{R} e^{-t/\tau}u(t)$$

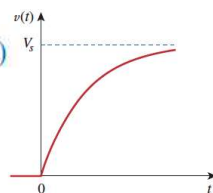


EHB 211E

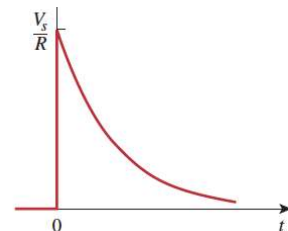

22

## Step Response of an RC Circuit

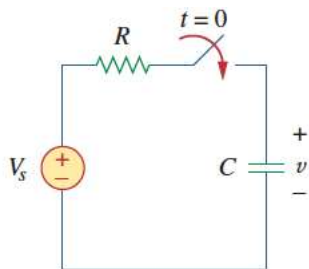

Complete response = natural response + forced response  
stored energy                      independent source

$$v = v_n + v_f$$

$$v_n = V_o e^{-t/\tau} \quad v_f = V_s (1 - e^{-t/\tau})$$

Alternative explanation:

Complete response = transient response + steady-state response  
temporary part                      permanent part

$$v = v_t + v_{ss}$$

$$v_t = (V_o - V_s) e^{-t/\tau} \quad v_{ss} = V_s$$

$$v(t) = v(\infty) + [v(0) - v(\infty)] e^{-t/\tau}$$

23

23

## Exercise

At  $t = 0$ , the switch moves from position A to B. Determine  $v(t)$  for  $t > 0$ .


$$v(0^-) = \frac{5}{5 + 3}(24) = 15 \text{ V}$$

$$v(0) = v(0^-) = v(0^+) = 15 \text{ V}$$

$$\tau = R_{Th}C = 4 \times 10^3 \times 0.5 \times 10^{-3} = 2 \text{ s}$$

$$v(\infty) = 30 \text{ V}$$

$$\begin{aligned} v(t) &= v(\infty) + [v(0) - v(\infty)] e^{-t/\tau} \\ &= 30 + (15 - 30) e^{-t/2} = (30 - 15e^{-0.5t}) \text{ V} \end{aligned}$$

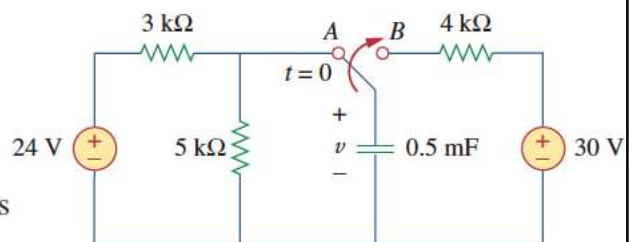

EHB 211E

24

24

## Exercise

At  $t = 0$ , the switch opens. Determine  $v(t)$  and  $i(t)$  for  $t > 0$ .

$$30u(t) = \begin{cases} 0, & t < 0 \\ 30, & t > 0 \end{cases}$$

$$v = 10 \text{ V}, \quad i = -\frac{v}{10} = -1 \text{ A}$$




$$v(0) = v(0^-) = 10 \text{ V}$$

$$v(\infty) = \frac{20}{20 + 10}(30) = 20 \text{ V}$$

$$R_{Th} = 10 \parallel 20 = \frac{10 \times 20}{30} = \frac{20}{3} \Omega$$

$$\tau = R_{Th}C = \frac{20}{3} \cdot \frac{1}{4} = \frac{5}{3} \text{ s}$$
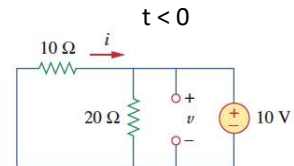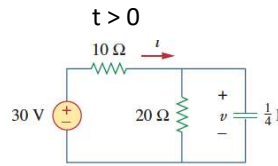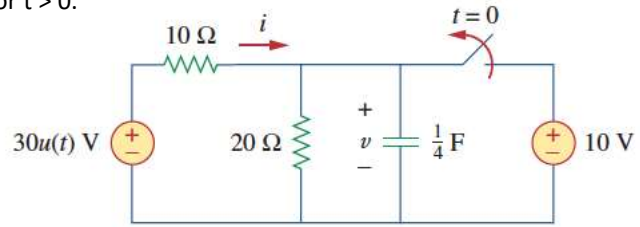
$$v(t) = v(\infty) + [v(0) - v(\infty)]e^{-t/\tau}$$



$$i = \frac{v}{20} + C \frac{dv}{dt} = (1 + e^{-0.6t}) \text{ A}$$

EHB 211E

25

25

## Step Response of an RL Circuit

The current response is the sum of transient and steady state responses:

$$i = i_t + i_{ss}$$



$$i_t = Ae^{-t/\tau}, \quad \tau = \frac{L}{R}$$

$$i_{ss} = \frac{V_s}{R}$$

$$i = Ae^{-t/\tau} + \frac{V_s}{R} \quad i(0^+) = i(0^-) = I_0$$

$$I_0 = A + \frac{V_s}{R} \Rightarrow A = I_0 - \frac{V_s}{R}$$

$$i(t) = \frac{V_s}{R} + \left(I_0 - \frac{V_s}{R}\right)e^{-t/\tau} \Rightarrow i(t) = i(\infty) + [i(0) - i(\infty)]e^{-t/\tau}$$

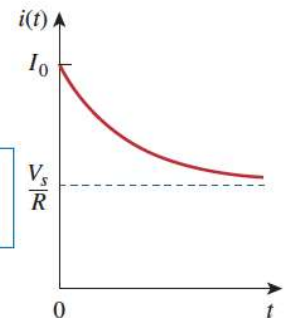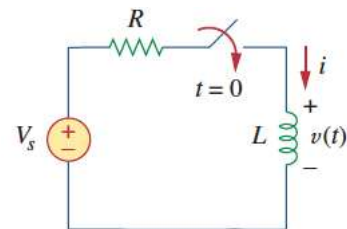

EHB 211E

26

26

## Exercise

Find  $i(t)$  for  $t > 0$ .


$$i(0^-) = \frac{10}{2} = 5 \text{ A}$$

$$i(0) = i(0^+) = i(0^-) = 5 \text{ A}$$

$$i(\infty) = \frac{10}{2+3} = 2 \text{ A}$$

$$R_{Th} = 2 + 3 = 5 \Omega \quad \tau = \frac{L}{R_{Th}} = \frac{\frac{1}{3}}{5} = \frac{1}{15} \text{ s}$$

$$i(t) = i(\infty) + [i(0) - i(\infty)]e^{-t/\tau} \\ = 2 + (5 - 2)e^{-15t} = 2 + 3e^{-15t} \text{ A}, \quad t > 0$$

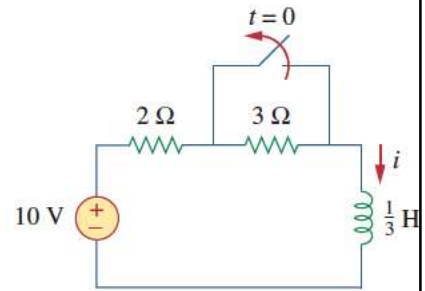

EHB 211E

27

27

## Exercise

At  $t = 0$ , switch 1 is closed.

At  $t = 4\text{s}$ , switch 2 is closed. Find  $i(t)$  for  $t > 0$ .

$$i(0^-) = i(0) = i(0^+) = 0$$

$$0 \leq t \leq 4$$

$$i(\infty) = \frac{40}{4+6} = 4 \text{ A}$$

$$R_{Th} = 4 + 6 = 10 \Omega \quad \tau = \frac{L}{R_{Th}} = \frac{5}{10} = \frac{1}{2}$$

$$i(t) = i(\infty) + [i(0) - i(\infty)]e^{-t/\tau} \\ = 4 + (0 - 4)e^{-2t} = 4(1 - e^{-2t}) \text{ A}, \quad 0 \leq t \leq 4$$

$$t \geq 4$$

$$i(4) = i(4^-) = 4(1 - e^{-8}) \approx 4 \text{ A}$$

Find the voltage ( $v$ ) at node P

$$\frac{40 - v}{4} + \frac{10 - v}{2} = \frac{v}{6} \Rightarrow v = \frac{180}{11} \text{ V} \quad i(\infty) = \frac{v}{6} = \frac{30}{11} = 2.727 \text{ A}$$

EHB 211E

28

28

## Exercise (continued)

At  $t = 0$ , switch 1 is closed.

At  $t = 4$ s, switch 2 is closed. Find  $i(t)$  for  $t > 0$ .

$$t \geq 4$$

$$i(4) = i(4^-) = 4(1 - e^{-8}) \approx 4 \text{ A}$$

Find the voltage( $v$ ) at node P

$$\frac{40 - v}{4} + \frac{10 - v}{2} = \frac{v}{6} \Rightarrow v = \frac{180}{11} \text{ V}$$


$$i(\infty) = \frac{v}{6} = \frac{30}{11} = 2.727 \text{ A}$$

$$R_{Th} = 4 \parallel 2 + 6 = \frac{4 \times 2}{6} + 6 = \frac{22}{3} \Omega \quad \tau = \frac{L}{R_{Th}} = \frac{5}{\frac{22}{3}} = \frac{15}{22} \text{ s}$$

$$i(t) = i(\infty) + [i(4) - i(\infty)]e^{-(t-4)/\tau}, \quad t \geq 4$$

$$i(t) = 2.727 + (4 - 2.727)e^{-(t-4)/\tau}, \quad \tau = \frac{15}{22}$$
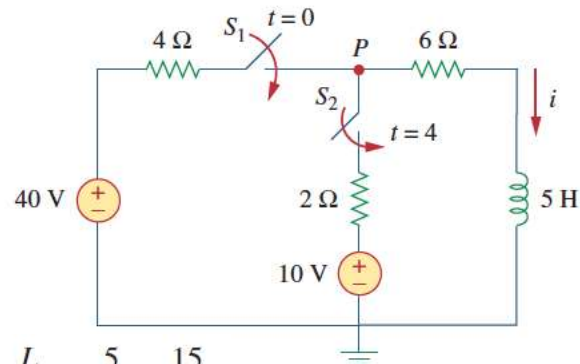
$$= 2.727 + 1.273e^{-1.4667(t-4)}, \quad t \geq 4$$



OVERALL

$$i(t) = \begin{cases} 0, & t \leq 0 \\ 4(1 - e^{-2t}), & 0 \leq t \leq 4 \\ 2.727 + 1.273e^{-1.4667(t-4)}, & t \geq 4 \end{cases}$$

29

## First-Order Op Amp Circuits - Exercise

For the op amp circuit, find  $v_o$  for  $t > 0$ , given that  $v(0) = 3$ V.  $R_f = 80$ k $\Omega$ ,  $R_1 = 20$ k $\Omega$ , and  $C = 5$  $\mu$ F.

### Method 1

$$\frac{0 - v_1}{R_1} = C \frac{dv}{dt} \quad \text{KCL at node 1}$$

$$v_1 = v$$

$$\frac{dv}{dt} + \frac{v}{CR_1} = 0 \quad (\text{same equation as source free RC circuit})$$


$$v(t) = V_0 e^{-t/\tau}, \quad \tau = R_1 C$$

$$v(0) = 3 = V_0 \quad \tau = 20 \times 10^3 \times 5 \times 10^{-6} = 0.1$$

$$v(t) = 3e^{-10t}$$

$$C \frac{dv}{dt} = \frac{0 - v_o}{R_f} \quad \text{KCL at node 2} \quad v_o = -R_f C \frac{dv}{dt}$$
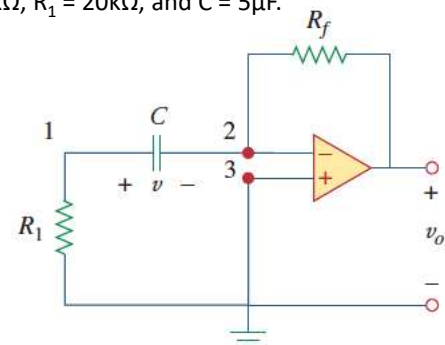
$$v_o = -80 \times 10^3 \times 5 \times 10^{-6} (-30e^{-10t}) = 12e^{-10t} \text{ V}$$



30

## First-Order Op Amp Circuits - Exercise

For the op amp circuit, find  $v_o$  for  $t > 0$ , given that  $v(0) = 3\text{V}$ ,  $R_f = 80\text{k}\Omega$ ,  $R_1 = 20\text{k}\Omega$ , and  $C = 5\mu\text{F}$ .

### Method 2

$$v(0^+) = v(0^-) = 3\text{ V}$$

KCL

$$\frac{3}{20,000} + \frac{0 - v_o(0^+)}{80,000} = 0 \quad v_o(0^+) = 12\text{ V}$$

Since the circuit is source free:  $v(\infty) = 0\text{ V}$

KVL at input loop to find  $R_{eq}$  observed by the capacitor.



Remove capacitor and place a 1A current source

$$20,000(1) - v = 0 \quad \Rightarrow \quad v = 20\text{ kV}$$

$$R_{eq} = \frac{v}{1} = 20\text{ k}\Omega \quad \tau = R_{eq}C = 0.1$$

$$\begin{aligned} v_o(t) &= v_o(\infty) + [v_o(0) - v_o(\infty)]e^{-t/\tau} \\ &= 0 + (12 - 0)e^{-10t} = 12e^{-10t}\text{ V}, \quad t > 0 \end{aligned}$$

EHB 211E

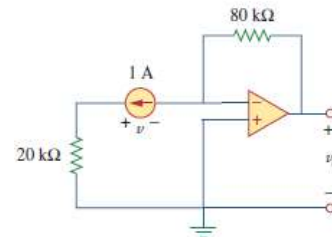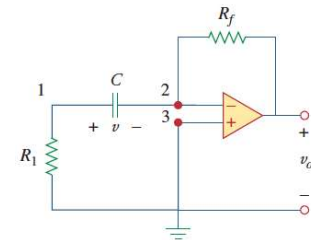

31