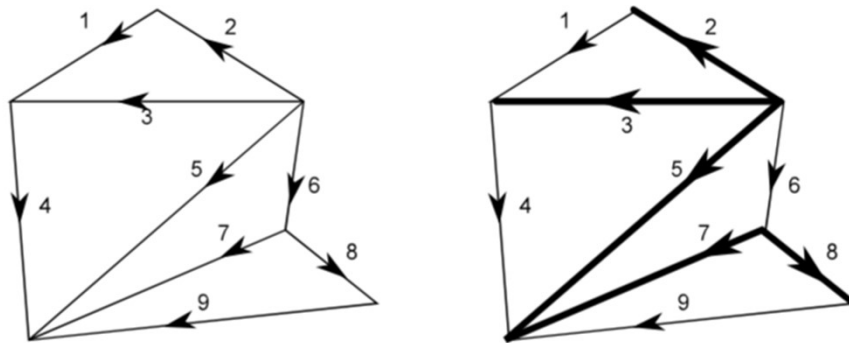


EHB 211E: Basics of Electrical Circuits *Graph Theory*

Asst. Prof. Ahmet Can Erten
(aerten@itu.edu.tr)

1

Example1 – Fundamental Cut-sets




Fundamental cut sets of the tree $G_T = \{2, 3, 5, 7, 8\}$ are $G_{C2} = \{2, 1\}$,
 $G_{C3} = \{3, 1, 4\}$, $G_{C5} = \{5, 4, 6\}$, $G_{C7} = \{7, 6, 9\}$, $G_{C8} = \{8, 9\}$.

EHB 211E

2

2

Example1 – Fundamental Cut-set Equations

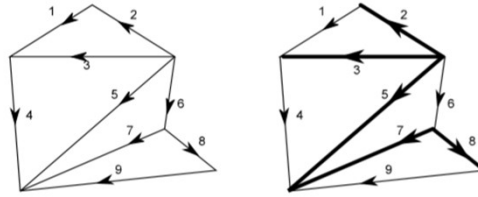


KCL equations based on Fundamental cut sets

$$\left[\begin{array}{cccc|cccccc} -1 & 0 & 0 & 0 & 1 & 0 & 0 & 0 & 0 \\ 1 & -1 & 0 & 0 & 0 & 1 & 0 & 0 & 0 \\ 0 & 1 & 1 & 0 & 0 & 0 & 1 & 0 & 0 \\ 0 & 0 & -1 & 1 & 0 & 0 & 0 & 1 & 0 \\ 0 & 0 & 0 & -1 & 0 & 0 & 0 & 0 & 1 \end{array} \right] \begin{array}{c} i_1 \\ i_4 \\ i_6 \\ i_9 \\ \hline i_2 \\ i_3 \\ i_5 \\ i_7 \\ i_8 \end{array} = 0$$

3

3

Example1 - Fundamental Loops

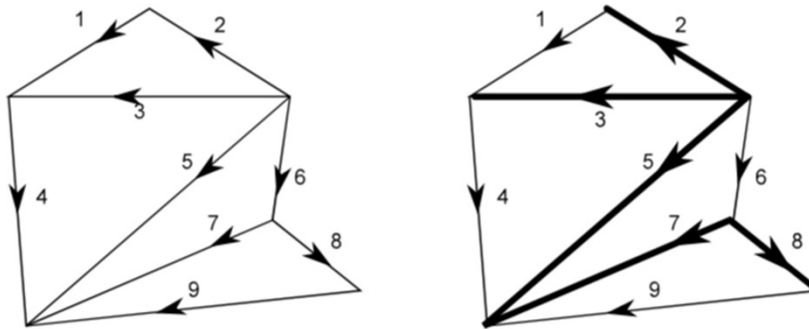


Fundamental Loop sets of the tree $G_T = \{2, 3, 5, 7, 8\}$ are $G_{L1} = \{1, 2, 3\}$, $G_{L4} = \{4, 3, 5\}$, $G_{L6} = \{6, 3, 7\}$, $G_{L9} = \{9, 7, 8\}$.

EHB 211E

4

4

Example1 - Fundamental Loop Equations

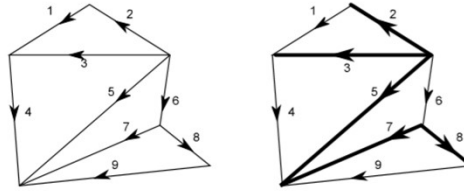

KVL equations based on the Fundamental loops


$$\left[\begin{array}{cccc|cccc} 1 & 0 & 0 & 0 & 1 & -1 & 0 & 0 & 0 \\ 0 & 1 & 0 & 0 & 0 & 1 & -1 & 0 & 0 \\ 0 & 0 & 1 & 0 & 0 & 0 & -1 & 1 & 0 \\ 0 & 0 & 0 & 1 & 0 & 0 & 0 & -1 & 1 \end{array} \right] \begin{bmatrix} V_1 \\ V_4 \\ V_6 \\ V_9 \\ - \\ V_2 \\ V_3 \\ V_5 \\ V_7 \\ V_8 \end{bmatrix} = 0$$

EHB 211E

5

5

Example1 – KVL Equations for the nodes

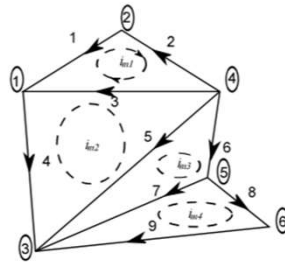

KVL equations for the nodes

$$\begin{bmatrix} V_1 \\ V_2 \\ V_3 \\ V_4 \\ V_5 \\ V_6 \\ V_7 \\ V_8 \\ V_9 \end{bmatrix} = \begin{bmatrix} -1 & 1 & 0 & 0 & 0 & 0 \\ 0 & -1 & 0 & 1 & 0 & 0 \\ -1 & 0 & 0 & 1 & 0 & 0 \\ 1 & 0 & -1 & 0 & 0 & 0 \\ 0 & 0 & -1 & 1 & 0 & 0 \\ 0 & 0 & 0 & 1 & -1 & 0 \\ 0 & 0 & -1 & 0 & 1 & 0 \\ 0 & 0 & 0 & 0 & 1 & -1 \\ 0 & 0 & 0 & 1 & 0 & 0 \end{bmatrix} \begin{bmatrix} V_{n1} \\ V_{n2} \\ V_{n3} \\ V_{n4} \\ V_{n5} \\ V_{n6} \end{bmatrix}$$

Prof. Dr. Mervat El-Sayed El-Din


Dr. El-Hod El-Din

Prof.

6

6

Example1 – KCL Equations for the nodes

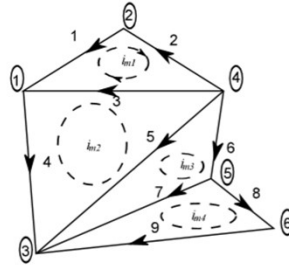


KCL equations for the nodes

$$\begin{bmatrix} -1 & 0 & -1 & 1 & 0 & 0 & 0 & 0 & 0 \\ 1 & -1 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & -1 & -1 & 0 & -1 & 0 & -1 \\ 0 & 1 & 1 & 0 & 1 & 1 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & -1 & 1 & 1 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 & -1 & 1 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \\ i_4 \\ i_5 \\ i_6 \\ i_7 \\ i_8 \\ i_9 \end{bmatrix} = 0$$

7

7

Example1 – Mesh Equations

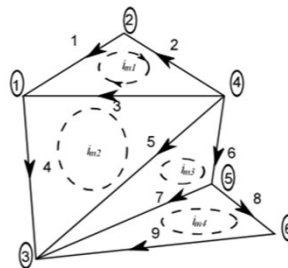

Mesh equations

$$\begin{bmatrix} i_1 \\ i_2 \\ i_3 \\ i_4 \\ i_5 \\ i_6 \\ i_7 \\ i_8 \\ i_9 \end{bmatrix} = \begin{bmatrix} -1 & 0 & 0 & 0 \\ -1 & 0 & 0 & 0 \\ 1 & -1 & 0 & 0 \\ 0 & -1 & 0 & 0 \\ 0 & 1 & -1 & 0 \\ 0 & 0 & 1 & 0 \\ 0 & 0 & 1 & -1 \\ 0 & 0 & 0 & 1 \\ 0 & 0 & 0 & 1 \end{bmatrix} \begin{bmatrix} i_{m1} \\ i_{m2} \\ i_{m3} \\ i_{m4} \end{bmatrix}$$

EMB 211E

8

8

Graph Theory : Chord Current Method

Solving linear circuits with two-terminal resistors / independent sources:



- 1) Pick a proper tree that includes voltage sources. Current sources are placed on co-trees.
- 2) Write fundamental loop equations, which do not correspond to current sources
- 3) Write v-i relations of the resistors in $v=r.i$ form
- 4) Substitute voltages found in step 3 -> equations found in step 2
- 5) Write fundamental cut-set equations that do not correspond to voltage sources
- 6) Substitute the fundamental loop equations in step 4 -> equations found in step 5
- 7) Present the equation in the form: $B i_l + Q i_s + M V_s = 0$

EHB 211E

9

9

Exercise

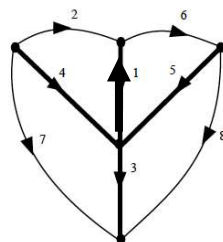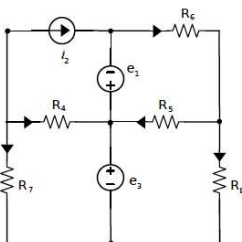

- 1) Pick a proper tree that includes voltage sources. Current sources are placed on co-trees.
- 2) Fundamental loop equations, which do not correspond to current sources

$$V_6 + V_5 + V_1 = 0$$

$$V_7 - V_4 - V_3 = 0$$

$$V_8 - V_3 - V_5 = 0$$

3-4) Write v-i relations of resistors and substitute

$$R_6 i_6 + R_5 i_5 + V_1 = 0$$

$$R_7 i_7 - R_4 i_4 - V_3 = 0$$

$$R_8 i_8 - V_3 - R_5 i_5 = 0$$

6) Substitute 5 into step 4

(all current are represented in terms of chord currents)

$$R_6 i_6 + R_5(-i_8 + i_6) + V_1 = 0$$

$$R_7 i_7 - R_4(-i_2 - i_7) - V_3 = 0$$

$$R_8 i_8 - V_3 - R_5(-i_8 + i_6) = 0$$

5) Fundamental cut-set equations

(that do not correspond to voltage sources)

$$i_4 + i_2 + i_7 = 0 \quad i_4 = -i_2 - i_7$$

$$i_5 + i_8 - i_6 = 0 \quad i_5 = -i_8 + i_6$$

$$\begin{bmatrix} i_1 \\ i_2 \\ i_3 \\ i_4 \\ i_5 \end{bmatrix} = \begin{bmatrix} -1 & 1 & 0 & 0 & 0 \\ 0 & 0 & 1 & -1 & 0 \\ -1 & 0 & 1 & 0 & 0 \\ 0 & 1 & 0 & -1 & 0 \end{bmatrix} \begin{bmatrix} i_6 \\ i_7 \\ i_8 \end{bmatrix}$$

$$\begin{bmatrix} R_6 + R_5 & 0 & -R_5 \\ 0 & R_7 + R_4 & 0 \\ -R_5 & 0 & R_8 + R_5 \end{bmatrix} \begin{bmatrix} i_6 \\ i_7 \\ i_8 \end{bmatrix} + \begin{bmatrix} 0 \\ R_4 \\ 0 \end{bmatrix} i_2 + \begin{bmatrix} 1 & 0 \\ 0 & -1 \\ 0 & -1 \end{bmatrix} \begin{bmatrix} V_1 \\ V_3 \end{bmatrix} = 0$$

EHB 211E

10

10

Graph Theory : Chord Current Method

Solving linear circuits with two-terminal resistors / independent sources:



- 1) Pick a proper tree that includes voltage sources. Current sources are placed on co-trees.
- 2) Write fundamental loop equations, which do not correspond to current sources
- 3) Write v-i relations of the resistors in $v=r.i$ form
- 4) Substitute voltages found in step 3 -> equations found in step 2
- 5) Write fundamental cut-set equations that do not correspond to voltage sources
- 6) Substitute the fundamental loop equations in step 4 -> equations found in step 5
- 7) Present the equation in the form: $B i_l + Q i_s + M V_s = 0$

EHB 211E

11

11

Exercise

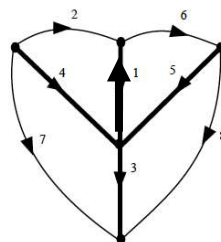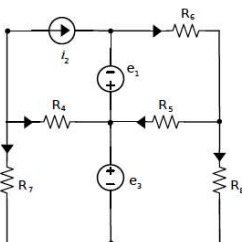

- 1) Pick a proper tree that includes voltage sources. Current sources are placed on co-trees.
- 2) Fundamental loop equations, which do not correspond to current sources

$$V_6 + V_5 + V_1 = 0$$

$$V_7 - V_4 - V_3 = 0$$

$$V_8 - V_3 - V_5 = 0$$

3-4) Write v-i relations of resistors and substitute

$$R_6 i_6 + R_5 i_5 + V_1 = 0$$

$$R_7 i_7 - R_4 i_4 - V_3 = 0$$

$$R_8 i_8 - V_3 - R_5 i_5 = 0$$

5) Fundamental cut-set equations
(that do not correspond to voltage sources)

$$\begin{aligned} i_4 + i_2 + i_7 &= 0 & i_4 &= -i_2 - i_7 \\ i_5 + i_8 - i_6 &= 0 & i_5 &= -i_8 + i_6 \end{aligned}$$

6) Substitute 5 into step 4

(all current are represented in terms of chord currents)

$$R_6 i_6 + R_5(-i_8 + i_6) + V_1 = 0$$

$$R_7 i_7 - R_4(-i_2 - i_7) - V_3 = 0$$

$$R_8 i_8 - V_3 - R_5(-i_8 + i_6) = 0$$

$$\begin{bmatrix} R_6 + R_5 & 0 & -R_5 \\ 0 & R_7 + R_4 & 0 \\ -R_5 & 0 & R_8 + R_5 \end{bmatrix} \begin{bmatrix} i_6 \\ i_7 \\ i_8 \end{bmatrix} + \begin{bmatrix} 0 \\ R_4 \\ 0 \end{bmatrix} i_2 + \begin{bmatrix} 1 & 0 \\ 0 & -1 \\ 0 & -1 \end{bmatrix} \begin{bmatrix} V_1 \\ V_3 \end{bmatrix} = 0$$

EHB 211E

12

12

Graph Theory : Generalized Chord Current Method

Solving linear circuits with two-terminal resistors / independent + dependent sources:



- Follow the same steps, treat dependent sources as independent sources
- Place the dependent voltage source in the tree, and within the co-tree if it is a current source.
- Using v-i relations of the dependent sources, new unknown variables are written in terms of link currents, voltage and current sources.

EHB 211E

13

13

Exercise

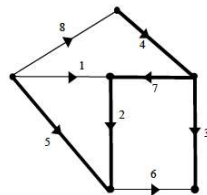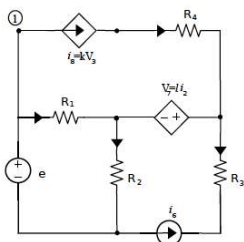

6) Substitute 5 into step 4

(all current are represented in terms of chord currents)

$$R_1 i_1 + R_2 (i_8 + i_1 + i_6) - e = 0$$

Express dependent source terms of independent source

$$i_8 = kV_3 \quad i_8 = kR_3 i_3$$

$$i_8 = -kR_3 i_6 \quad \text{Write in terms of link current (i3 term is replaced by i6 term)}$$

$$(R_1 + R_2) i_1 + (R_2 - kR_3) i_6 - e = 0$$

If the circuit contains multi-terminal elements -> consider it as an independent source

1) Pick a proper tree that includes voltage sources.
Current sources are placed on co-trees.

2) Fundamental loop equations,
which do not correspond to current sources (link 1)

$$V_1 + V_2 - V_5 = 0$$

3-4) Find v-i relations of resistors

$$R_1 i_1 + R_2 i_2 - e = 0$$

5) Fundamental cut-set equations

(that do not correspond to voltage sources)

$$i_2 - i_8 - i_1 - i_6 = 0$$

EHB 211E

14

14

Graph Theory : Branch voltages method

Solving linear circuits with two-terminal resistors

- 1) Pick a proper tree that includes voltage sources. Current sources are placed on co-trees.
- 2) Write fundamental cut-set equations for the branches (exclude branches having voltage sources)
- 3) Write v-i relations of the resistors in $i=g.k$ form
- 4) Substitute the currents found in step 3 -> equations found in step 2
- 5) Write fundamental loop equations that do not correspond to links having current sources
- 6) Substitute the fundamental loop equations in step 5 -> equations found in step 4
- 7) Present the equation in the form:



$$MV_{b'} + Qi_s + Mv_s = 0$$

EHB 211E

15

15

Exercise

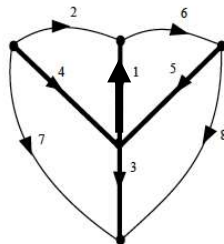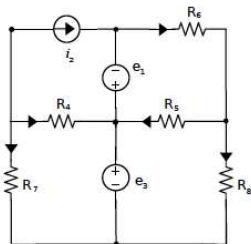

5) Fundamental loop equations, without current sources

$$\begin{aligned} V_6 + V_5 + V_1 &= 0 & V_6 &= -V_5 - V_1 \\ V_7 - V_4 - V_3 &= 0 & V_7 &= V_4 + V_3 \\ V_8 - V_3 - V_5 &= 0 & V_8 &= V_3 + V_5 \end{aligned}$$

Chord voltages from branch voltages

$$\begin{bmatrix} V_2 \\ V_6 \\ V_7 \\ V_8 \end{bmatrix} = \begin{bmatrix} 1 & 0 & 1 & 0 \\ -1 & 0 & 0 & -1 \\ 0 & -1 & -1 & 0 \\ 0 & 1 & 0 & 1 \end{bmatrix} \begin{bmatrix} V_1 \\ V_3 \\ V_4 \\ V_5 \end{bmatrix} \leftarrow \begin{bmatrix} G_4 - G_7 & 0 \\ 0 & G_5 + G_6 + G_8 \end{bmatrix} \begin{bmatrix} V_4 \\ V_5 \end{bmatrix} + \begin{bmatrix} 0 & -G_7 \\ G_6 & G_8 \end{bmatrix} \begin{bmatrix} V_1 \\ V_3 \end{bmatrix} + \begin{bmatrix} 1 \\ 0 \end{bmatrix} i_2 = 0$$

EHB 211E

16

16

- 1) Pick a proper tree that includes voltage sources. Current sources are placed on co-trees.
- 2) Fundamental cut set equations for branches 4-5 which do not correspond to voltage sources

$$i_4 + i_2 + i_7 = 0$$

$$i_5 - i_6 + i_8 = 0$$

- 3-4) Write i-v relations of resistors and replace into 2

$$G_4 V_4 + i_2 + G_7 V_7 = 0$$

$$G_5 V_5 - G_6 V_6 + G_8 V_8 = 0$$

$$\begin{aligned} &\downarrow \\ G_4 V_4 + i_2 - G_7 (V_4 + V_3) &= 0 \\ G_5 V_5 - G_6 (-V_5 - V_1) + G_8 (V_3 + V_5) &= 0 \end{aligned}$$

(everything is represented in terms of branch voltages)

Graph Theory : Nodal Analysis

Solving linear circuits with two-terminal resistors

- 1) Draw the circuit graph and choose a reference node which is connected to the maximum number of voltage sources.
- 2) Write fundamental cut-set equations for the nodes which do not correspond to node of a voltage sources.
- 3) Write v-i relations of the resistors in $i=g.V$ form
- 4) V is written in terms of node voltages.
- 5) Present the equation in the form:


$$A_{11} G_R A_{11}^T V_d + A_{12} i_k = 0$$

EHB 211E

17

17

Exercise

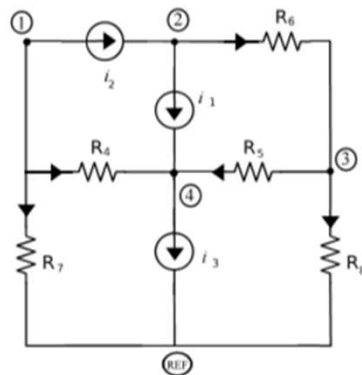

2. The fundamental cut-set equations for the nodes:

$$\begin{aligned} i_4 + i_2 + i_7 &= 0 \\ i_1 + i_6 - i_2 &= 0 \\ i_5 - i_6 + i_8 &= 0 \\ i_3 - i_1 - i_5 - i_4 &= 0 \end{aligned}$$

3. Resistors in the circuit:

$$i_k = G_k V_k \quad k = \{4, 5, 6, 7, 8\}$$

4. Substitute terminal equations of the resistors into the previous equation

$$\begin{aligned} G_4 V_4 + i_2 + G_7 V_7 &= 0 \\ i_1 - G_6 V_6 - i_2 &= 0 \\ G_5 V_5 - G_6 V_6 + G_8 V_8 &= 0 \\ i_3 - i_1 - G_5 V_5 - G_4 V_4 &= 0 \end{aligned}$$

5. Terminal voltage is written in terms of the node voltages:

$$\begin{aligned} V_1 &= \cdot \\ V_2 &= \cdot \\ V_3 &= \cdot \\ V_4 &= \cdot \\ V_5 &= \cdot \\ V_6 &= \cdot \\ V_7 &= \cdot \\ V_8 &= \cdot \end{aligned}$$

EHB 211E

18

18

Exercise

6. Substitute the equation in step 5 into step 4

$$\begin{aligned} G_4(V_{d1} - V_{d4}) + i_2 + G_7 V_{d1} &= 0 \\ i_1 - G_6(V_{d2} - V_{d3}) - i_2 &= 0 \\ G_5(V_{d3} - V_{d4}) - G_6(V_{d2} - V_{d3}) + G_8 V_{d3} &= 0 \\ i_3 - i_1 - G_5(V_{d3} - V_{d4}) - G_4(V_{d1} - V_{d4}) &= 0 \end{aligned}$$

Equations are presented in the matrix form


$$\begin{bmatrix} G_4 + G_7 & 0 & 0 & -G_4 \\ 0 & G_6 & -G_6 & 0 \\ 0 & -G_6 & G_5 + G_6 + G_8 & -G_5 \\ -G_4 & 0 & -G_5 & G_4 + G_5 \end{bmatrix} \begin{bmatrix} V_{d1} \\ V_{d2} \\ V_{d3} \\ V_{d4} \end{bmatrix} + \begin{bmatrix} 0 & 1 & 0 \\ 1 & -1 & 0 \\ 0 & 0 & 0 \\ -1 & 0 & 1 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} = 0$$

EHB 211E

19

19

Exercise – Generalized Nodal Analysis

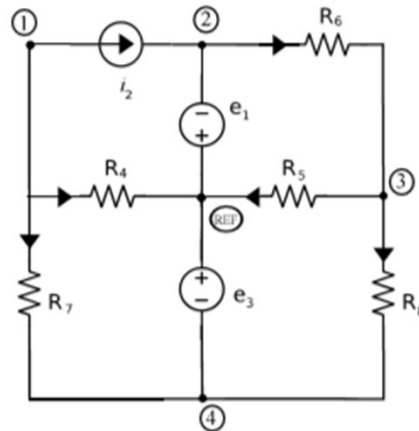

2. the fundamental cut-set equations for the nodes

$$\begin{aligned} i_4 + i_2 + i_7 &= 0 \\ i_5 - i_6 + i_8 &= 0 \end{aligned}$$

3. Write the $v - i$ relations of the resistors:

$$i_k = G_k V_k \quad k = \{4, 5, 6, 7, 8\}$$

4. Substitute the equations in Step 3 into the equations in Step 2.

$$\begin{aligned} G_4 V_4 + i_2 + G_7 V_7 &= 0 \\ G_5 V_5 - G_6 V_6 + G_8 V_8 &= 0 \end{aligned}$$

5. Terminal voltage is written in terms of the node voltages:

$$\begin{aligned} V_1 &= -V_{d2} \\ V_2 &= V_{d1} - V_{d2} \\ V_3 &= -V_{d4} \\ V_4 &= V_{d1} \\ V_5 &= V_{d3} \\ V_6 &= V_{d2} - V_{d3} \\ V_7 &= V_{d4} - V_{d1} \\ V_8 &= V_{d3} - V_{d4} \end{aligned}$$

EHB 211E

20

20

Exercise - Generalized Nodal Analysis

6. Substitute the equation in step 5 into step 4:

$$\begin{aligned} G_4 V_{d1} + i_2 + G_7(V_{d4} - V_{d1}) &= 0 \\ G_5 V_{d3} - G_6(V_{d2} - V_{d3}) + G_8(V_{d3} - V_{d4}) &= 0 \end{aligned}$$

Voltage sources are written in the terms of the node voltages

$$\begin{aligned} V_{d2} &= -e_1 \\ V_{d4} &= -e_3 \end{aligned}$$

Equations are presented in the matrix form:

$$\begin{bmatrix} G_4 - G_7 & 0 \\ 0 & G_5 + G_6 + G_8 \end{bmatrix} \begin{bmatrix} V_{d1} \\ V_{d3} \end{bmatrix} + \begin{bmatrix} 1 \\ 0 \end{bmatrix} i_2 + \begin{bmatrix} 0 & -G_7 \\ G_6 & G_8 \end{bmatrix} \begin{bmatrix} e_1 \\ e_3 \end{bmatrix} = 0$$

EHB 211E

21

21

Graph Theory : Loop (Mesh) Current Method

- ① Draw the circuit graph and assign the loop currents.
- ② Write mesh equations are obtained from KVL which is applied to each of the loop: $Bv = 0$ It can also be written such as

$$Bv = B_1 v_R + B_2 v_k = 0$$

where v_k and v_R voltages of independent voltage sources and resistors, respectively.

- ③ Write the ohm law for the resistors: $v_R = \mathbf{R}i_R$
- ④ Substitute the equations in Step 3 into the equations in Step 2.

$$[B_1 \ B_2]v = B_1 \mathbf{R}i_R + B_2 v_k = 0$$

- ⑤ Resistors's currents are written in terms of the mesh currents:

$$i_R = B_1^T i_c$$


- ⑥ Substitute the equation in step 5 into step 4:

EHB 211E

22

22

Exercise

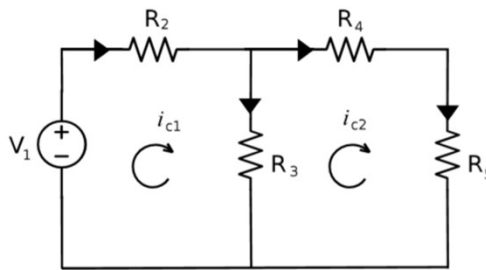

2. Mesh equations:

$$\begin{aligned} V_2 + V_3 - V_1 &= 0 \\ V_4 + V_5 - V_3 &= 0 \end{aligned}$$

3. Substitute the $v_R = Ri_R$ equations into the equations in Step 2:

$$\begin{aligned} R_2 i_2 + R_3 i_3 - V_1 &= 0 \\ R_4 i_4 + R_5 i_5 - R_3 i_3 &= 0 \end{aligned}$$

4. Resistors's currents are written in terms of the mesh currents:

$$\begin{aligned} i_2 &= i_{c1} \\ i_3 &= i_{c1} - i_{c2} \\ i_4 &= i_{c2} \\ i_5 &= i_{c2} \end{aligned}$$

5. Substitute the equation in step 4 into step 3:

$$\begin{aligned} R_2 i_{c1} + R_3(i_{c1} - i_{c2}) - V_1 &= 0 \\ R_4 i_{c2} + R_5 i_{c2} - R_3(i_{c1} - i_{c2}) &= 0 \end{aligned}$$

6. In matrix form:


$$\begin{bmatrix} R_2 + R_3 & -R_3 \\ -R_3 & R_3 + R_4 + R_5 \end{bmatrix} \begin{bmatrix} i_{c1} \\ i_{c2} \end{bmatrix} + \begin{bmatrix} -1 \\ 0 \end{bmatrix} V_1 = 0$$

EHB 211E

23

23

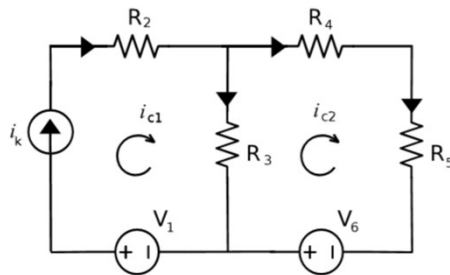Exercise - Generalized Mesh Current Analysis



2. Mesh equations:

$$\begin{aligned} V_2 + V_3 - V_1 + V_k &= 0 \\ V_4 + V_5 - V_6 - V_3 &= 0 \end{aligned}$$

3. Substitute the $v_R = Ri_R$ equations into the equations in Step 2:

$$\begin{aligned} R_2 i_2 + R_3 i_3 - V_1 + V_k &= 0 \\ R_4 i_4 + R_5 i_5 - V_6 - R_3 i_3 &= 0 \end{aligned}$$

4. Resistors's currents are written in terms of the mesh currents:

$$\begin{aligned} i_2 &= i_{c1} \\ i_3 &= i_{c1} - i_{c2} \\ i_4 &= i_{c2} \\ i_5 &= i_{c2} \end{aligned}$$

5. Substitute the equation in step 5 into step 4:

$$\begin{aligned} R_2 i_{c1} + R_3(i_{c1} - i_{c2}) - V_1 + V_k &= 0 \\ R_4 i_{c2} + R_5 i_{c2} - V_6 - R_3(i_{c1} - i_{c2}) &= 0 \end{aligned}$$

Additional equation:

$$i_k = i_{c1}$$

6. Unknown mesh current:

$$(R_4 + R_5 + R_3)i_{c2} - R_3 i_k - V_6 = 0$$

EHB 211E

24

24