

EHB211E Basics of Electrical Circuits

HOMEWORK 2

For the Spice solutions, provide the schematic showing the voltage and current values and the output file.

- 1) For the bridge network in Figure 1, find i_o using mesh analysis. Also, obtain and show these values using PSpice program.

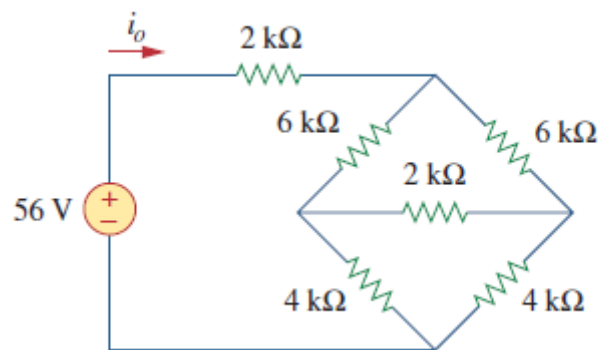


Figure 1

- 2) Find V_1 and V_2 using nodal analysis in Figure 2. Also, obtain and show the voltage values using PSpice program.

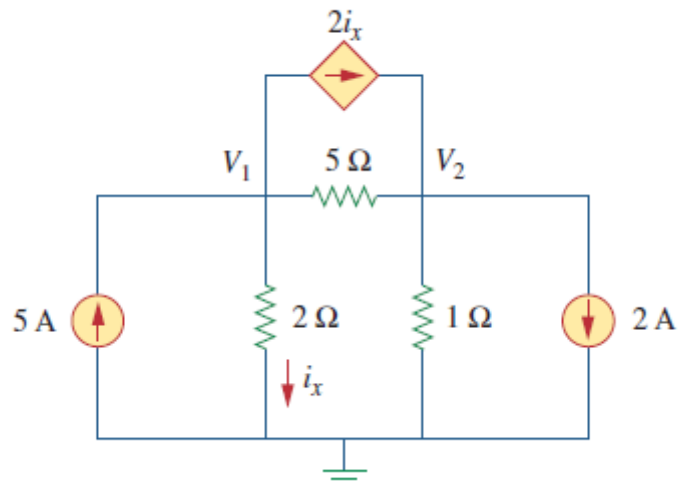


Figure 2

- 3) For the circuit in Figure 3, find the Thevenin equivalent between terminals a and b. Also, find and show V_{TH} and R_{TH} values using PSpice program.

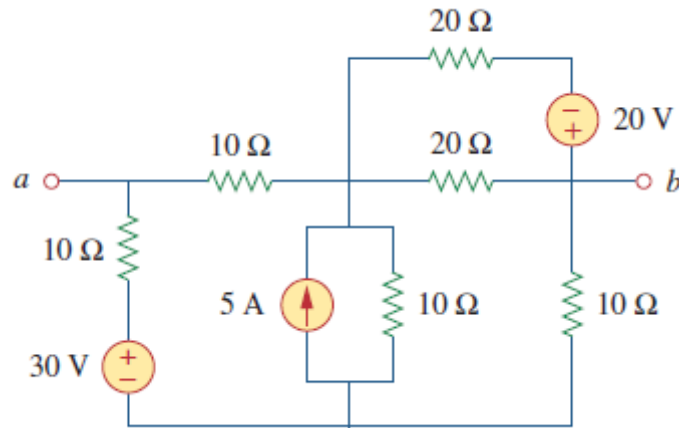


Figure 3

- 4) Given the circuit in Figure 4, obtain the Norton equivalent as viewed from terminals listed below. Also, find and show I_N and R_N values using PSpice program.

(a) a-b

(b) c-d

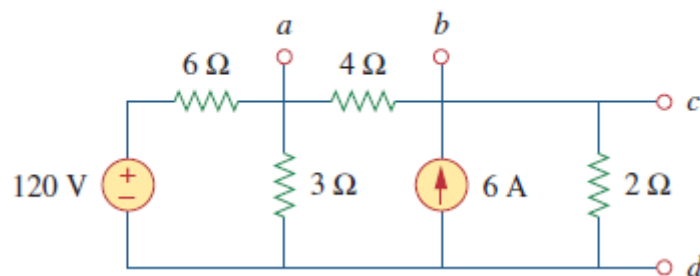


Figure 4

- 5) Calculate v_o in the op amp circuit of Figure 5 assuming all op amps are ideal. Also, obtain and show v_o using PSpice program.

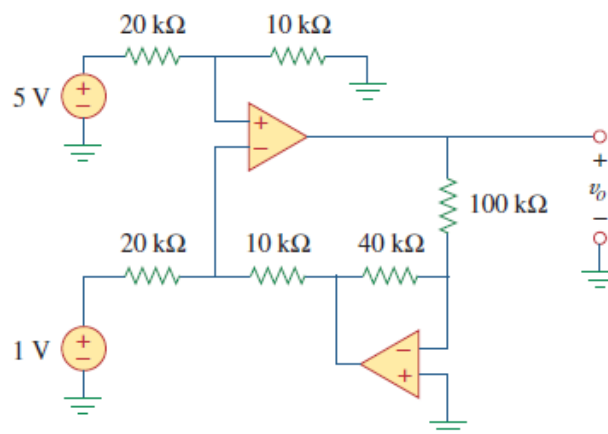


Figure 5

- 6) Calculate i_o in the op amp circuit of Figure 8 assuming all op amps are ideal. Also, obtain and show i_o using PSpice program.

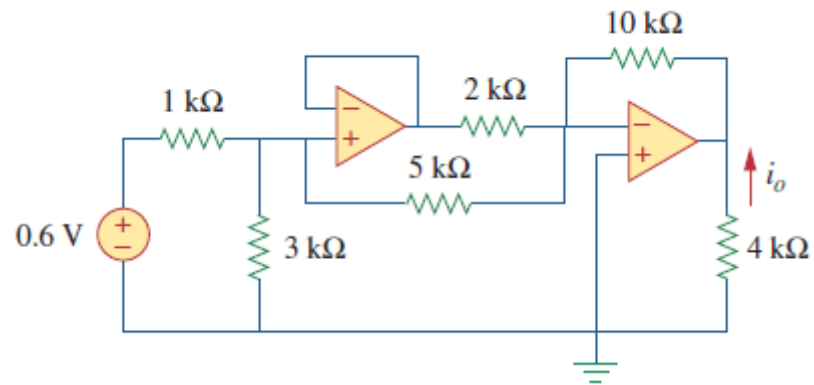


Figure 6