

EHB 211E: Basics of Electrical Circuits

Circuit Theorems


Asst. Prof. Ahmet Can Erten
(aerten@itu.edu.tr)

TA: Merve Gulle (gullem@itu.edu.tr)

1

Thevenin's Theorem

- A particular element in a circuit is variable (load) while other elements are fixed.
Example: A household outlet terminal may be connected to different appliances constituting a variable load.
- Each time the variable element is changed, the entire circuit has to be analyzed all over again.
- To avoid this problem, Thevenin's Theorem provides a technique by which the fixed part of the circuit is replaced by an equivalent, simplified circuit.

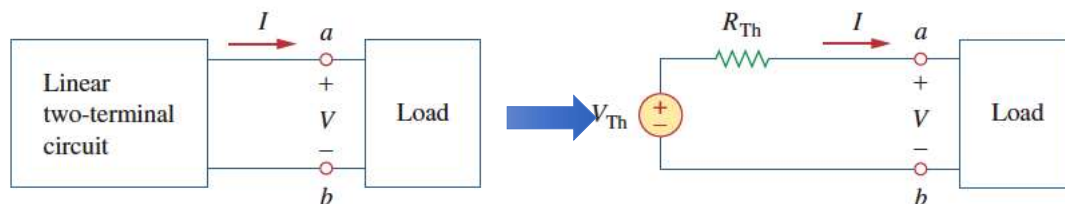


Thevenin's theorem states that a linear time-invariant resistive two-terminal one-port circuit can be replaced by an equivalent circuit consisting of a voltage source (V_{Th}) in series with a resistor (R_{Th}), where V_{Th} is the open circuit voltage at the terminals and R_{Th} is the input / equivalent resistance at the terminals when the independent sources are turned off.

EHB 211E

2

2

Thevenin's Theorem - *summary*

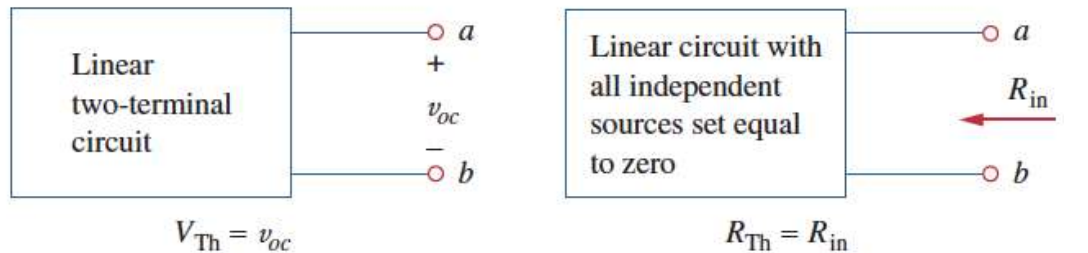

$$i_o = (v_o - v_{Th}) / R_{Th}$$

-> 0 intercept of the below graph gives v_{Th}


-> slope gives R_{Th}

EHB 211E


3

Thevenin's Theorem – *two cases*

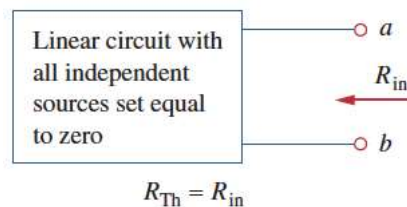
- CASE 1: If the circuit has no dependent sources, we turn off all independent sources, R_{Th} is the input resistance of the network looking between terminals a-b.



- CASE 2: If the network has dependent sources, we turn off all independent sources (similar to superposition principle the dependent sources stay). We apply a voltage source (v_o) at terminals a-b, and determine the resulting current (i_o). Then: $R_{Th} = v_o / i_o$

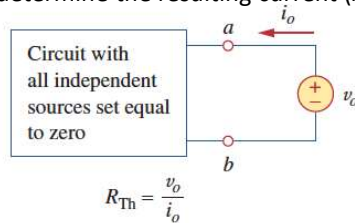

EHB 211E

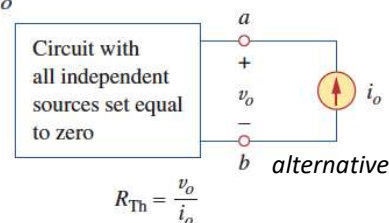

4


4

Thevenin's Theorem – *benefits*

- Greatly simplifies the circuit! A large circuit is replaced by an independent source and a resistor.
- The equivalent circuit behaves the same way as the original circuit.
- Consider a linear circuit terminated by a load resistance, current through the node, and the voltage across the terminal can be calculated by:

$$I_L = \frac{V_{Th}}{R_{Th} + R_L}$$

$$V_L = R_L I_L = \frac{R_L}{R_{Th} + R_L} V_{Th}$$

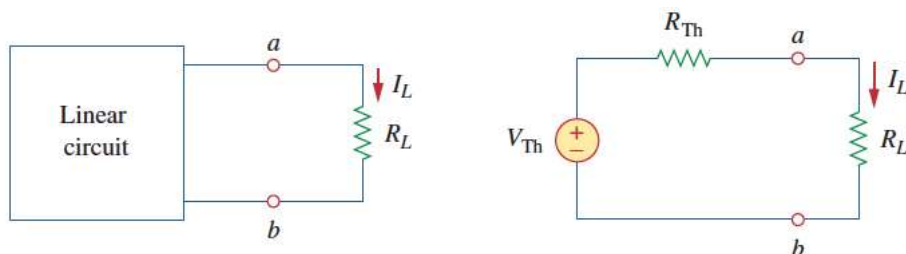


EHB 211E

5

5

Exercise

Find the Thevenin equivalent for the circuit below, to the left of terminals a-b. Then, find the current for $R_L = 6, 16 \Omega$

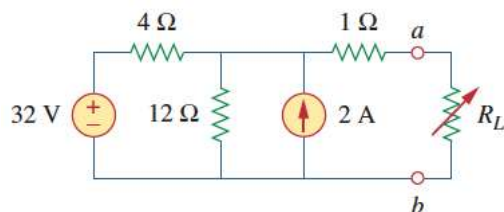


EHB 211E

6

6

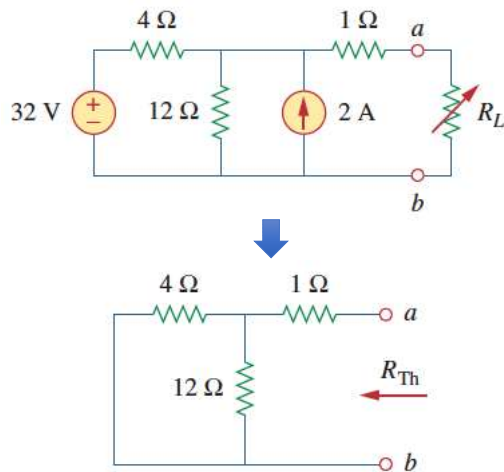
Exercise

Find the Thevenin equivalent for the circuit below, to the left of terminals a-b. Then, find the current for $R_L = 6, 16 \Omega$



$$R_{Th} = 4 \parallel 12 + 1 = \frac{4 \times 12}{16} + 1 = 4 \Omega$$

To find V_{Th} , apply mesh analysis

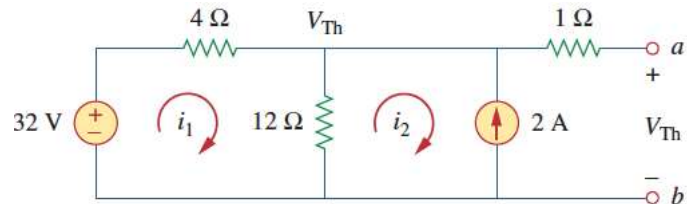

$$-32 + 4i_1 + 12(i_1 - i_2) = 0, \quad i_2 = -2 \text{ A}$$

$$i_1 = 0.5 \text{ A}$$

$$V_{Th} = 12(i_1 - i_2) = 12(0.5 + 2.0) = 30 \text{ V}$$


EHB 211E

7

7

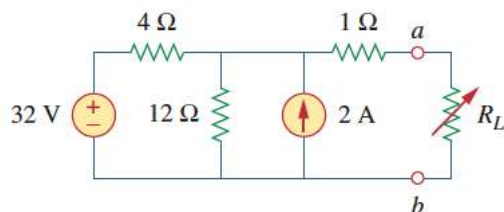Exercise (continued...)

Find the Thevenin equivalent for the circuit below, to the left of terminals a-b. Then, find the current for $R_L = 6, 16 \Omega$



Alternatively use nodal analysis,


EHB 211E

8

8

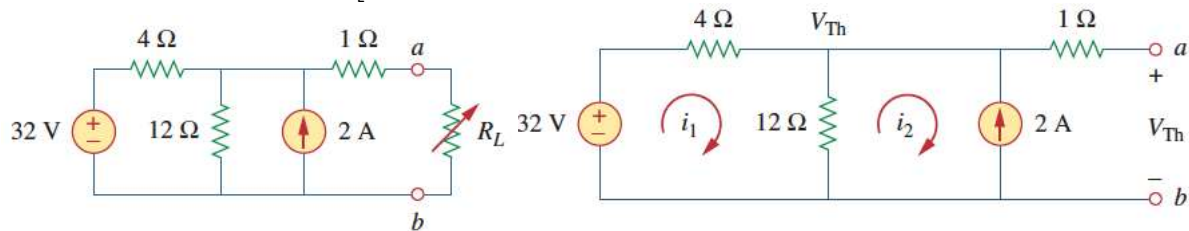Exercise (continued...)

Find the Thevenin equivalent for the circuit below, to the left of terminals a-b. Then, find the current for $R_L = 6, 16 \Omega$




Alternatively use nodal analysis,

$$\frac{32 - V_{Th}}{4} + 2 = \frac{V_{Th}}{12} \Rightarrow V_{Th} = 30 \text{ V}$$

$$I_L = \frac{V_{Th}}{R_{Th} + R_L} = \frac{30}{4 + R_L}$$

$$I_L = \frac{30}{10} = 3 \text{ A} \quad R_L = 6 \quad I_L = \frac{30}{20} = 1.5 \text{ A} \quad R_L = 16$$

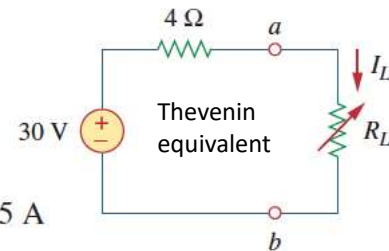


EHB 211E

9

9

Exercise

Find the Thevenin equivalent for the circuit below, at terminals a-b.

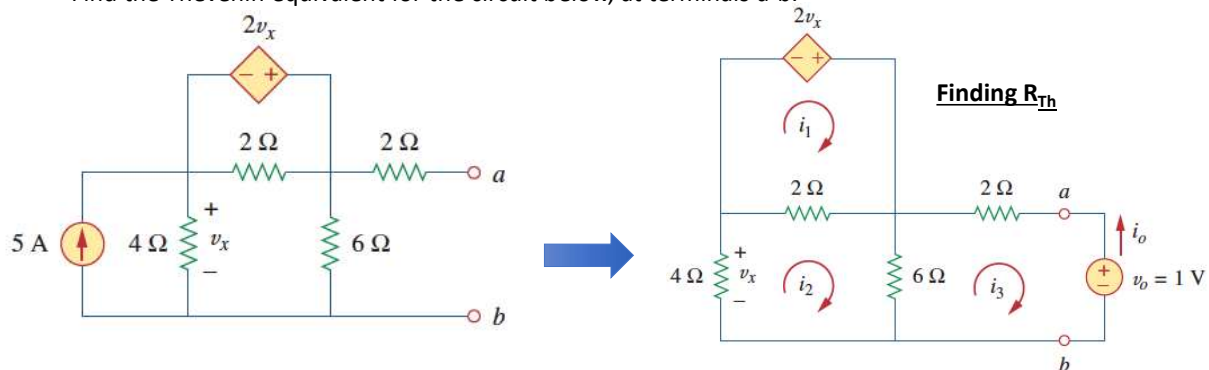


EHB 211E

10

10

Exercise

Find the Thevenin equivalent for the circuit below, at terminals a-b.

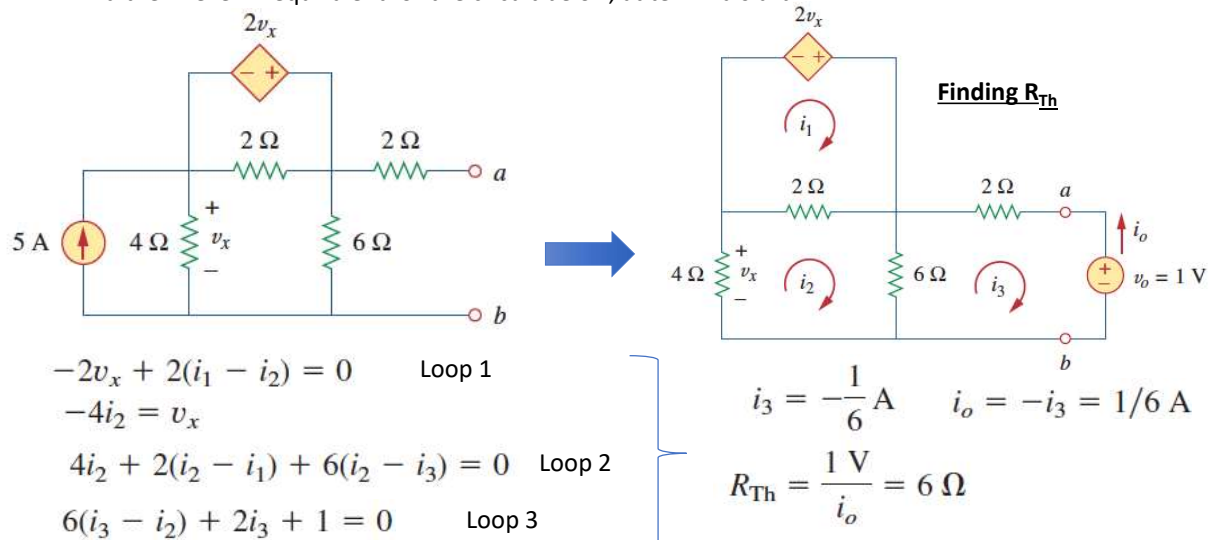


EHB 211E

11

11

Exercise (continued)

Find the Thevenin equivalent for the circuit below, at terminals a-b.

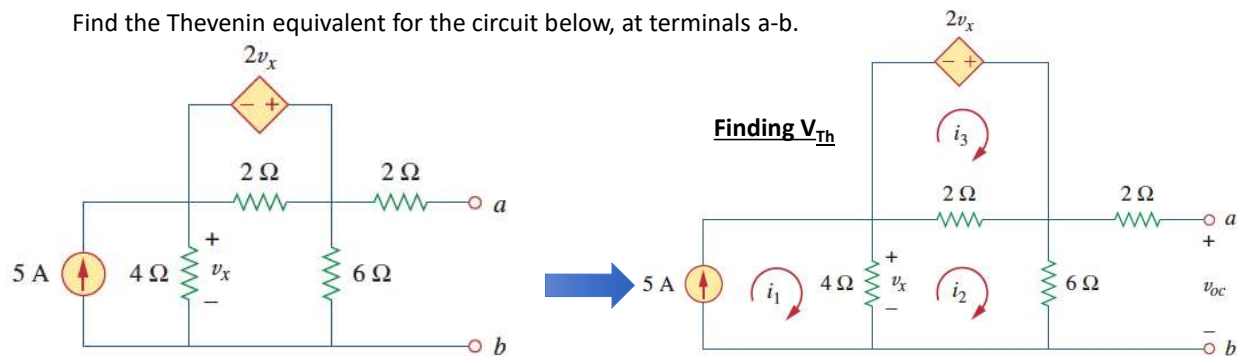


EHB 211E

12

12

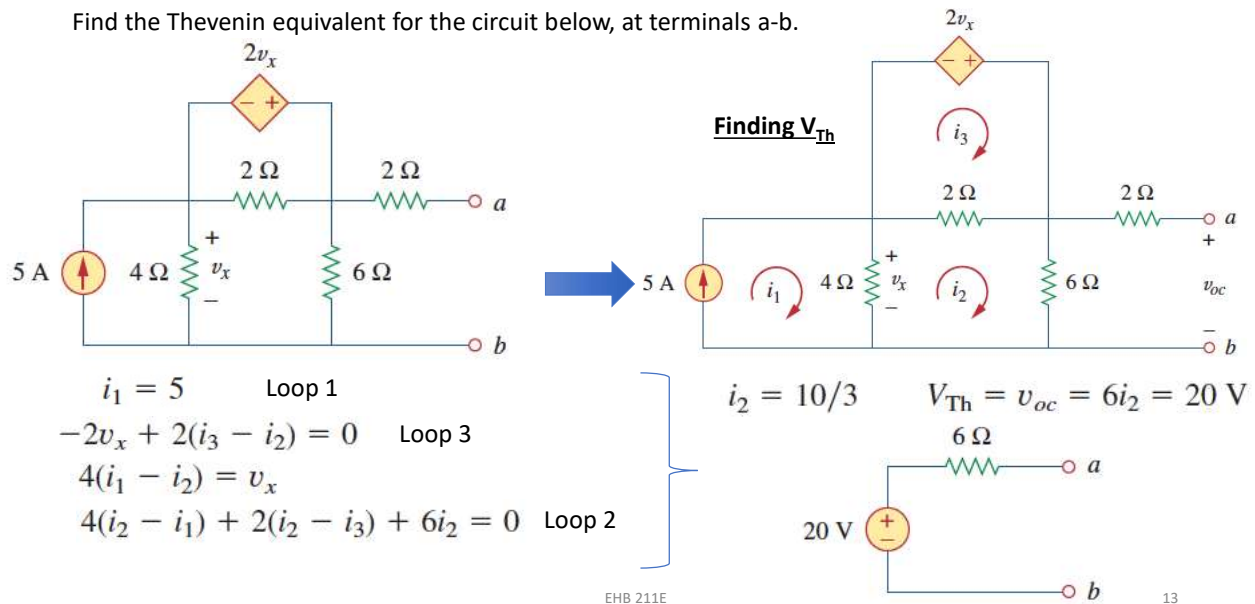Exercise (continued)


Find the Thevenin equivalent for the circuit below, at terminals a-b.



13

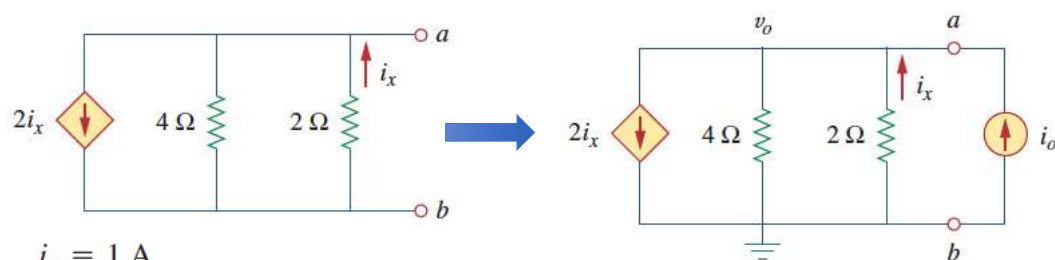Exercise


Find the Thevenin equivalent for the circuit below, at terminals a-b.



14

Norton's Theorem

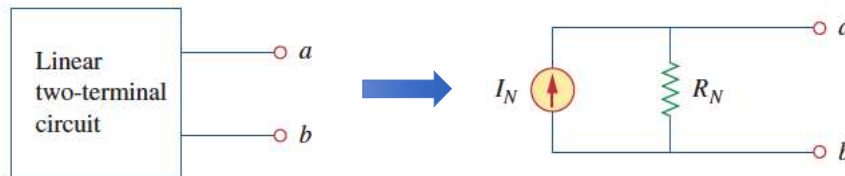Norton's theorem states that a linear time-invariant resistive two-terminal one-port circuit can be replaced by an equivalent circuit consisting of a current source (I_N) in parallel with a resistor (R_N), where I_N is the short circuit current at the terminals and R_N is the input / equivalent resistance at the terminals when the independent sources are turned off.



From source transformation:

$$R_N = R_{Th}$$

$$I_N = \frac{V_{Th}}{R_{Th}}$$

$$I_N = i_{sc}$$


EHB 211E

15

15

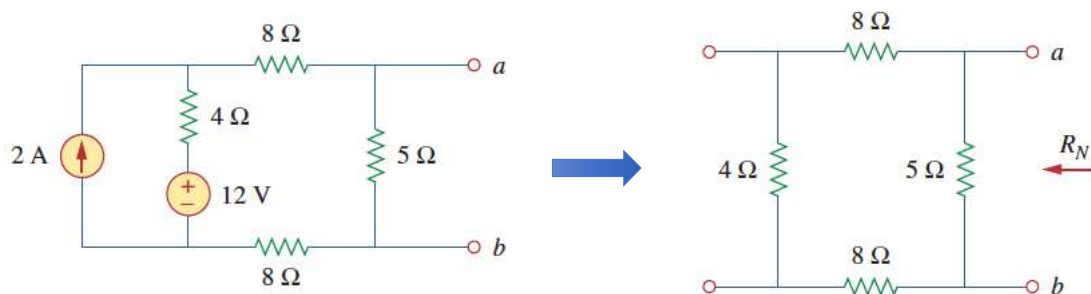Exercise

Find the Norton equivalent for the circuit below, at terminals a-b.



Finding R_N

$$R_N = 5 \parallel (8 + 4 + 8) = 5 \parallel 20 = \frac{20 \times 5}{25} = 4 \Omega$$


EHB 211E

16

16

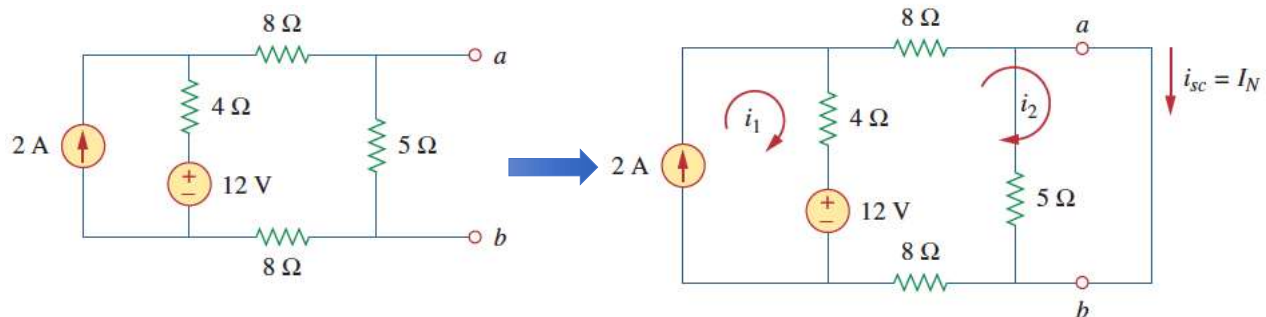Exercise (continued...)

Find the Norton equivalent for the circuit below, at terminals a-b.



Finding I_N

$$i_1 = 2 \text{ A}, \quad 20i_2 - 4i_1 - 12 = 0$$

$$i_2 = 1 \text{ A} = i_{sc} = I_N$$


EHB 211E

17

17

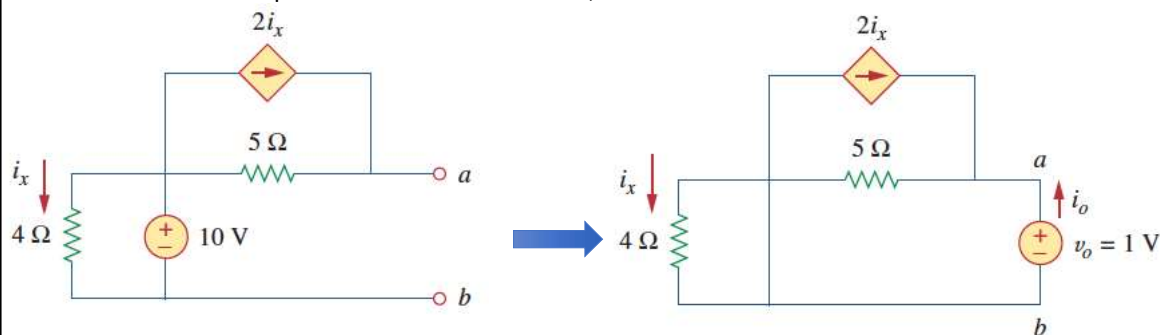Exercise

Find the Norton equivalent for the circuit below, at terminals a-b.



Finding R_N

No current passes on 4Ω :

-> $i_x = 0$

-> Dependent source is open circuited

$$i_o = \frac{1v}{5\Omega} = 0.2 \text{ A} \quad v_o = 1 \text{ V}$$

$$R_N = \frac{v_o}{i_o} = \frac{1}{0.2} = 5 \Omega$$


EHB 211E

18

18

Exercise

Find the Norton equivalent for the circuit below, at terminals a-b.

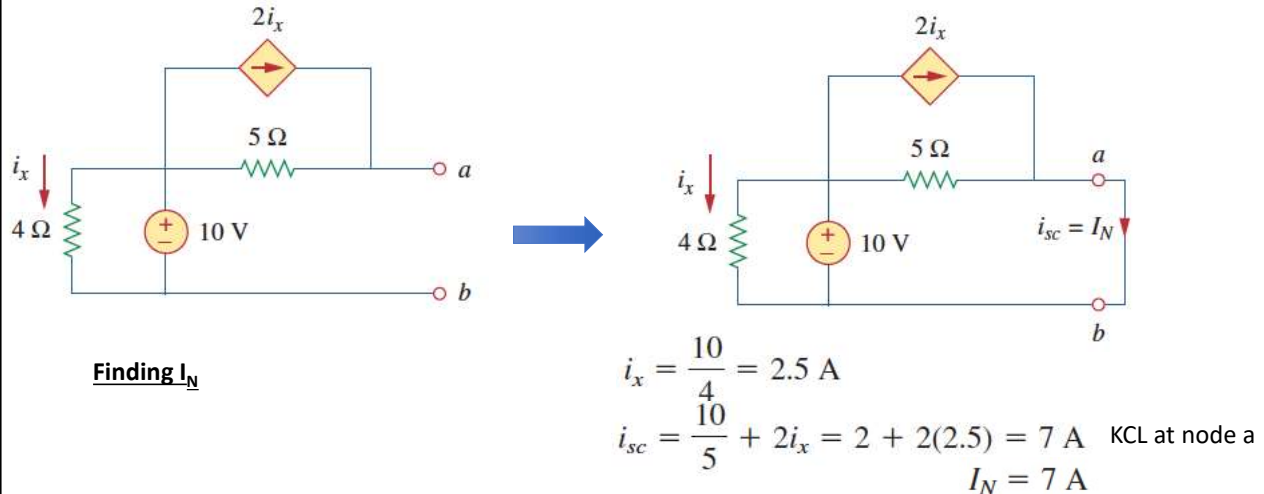


EHB 211E

19

19

Maximum Power Transfer

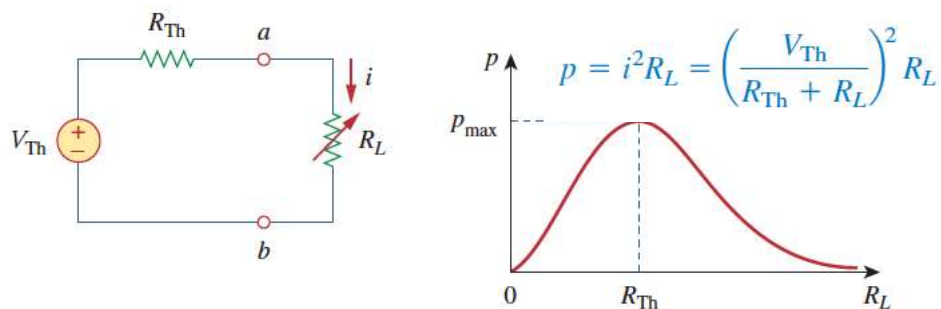For many applications, circuits are designed to deliver power to the load.
It is desirable to maximize the power, delivered to the load:



Maximum power is transferred to the load, when the load resistance equals the Thevenin resistance, seen from the load


EHB 211E

20

20

Maximum Power Transfer - proof

$$p = i^2 R_L = \left(\frac{V_{Th}}{R_{Th} + R_L} \right)^2 R_L$$

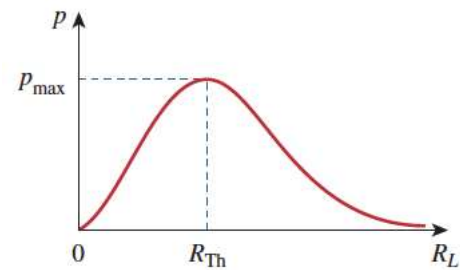

EHB 211E

21

21

Maximum Power Transfer - proof


$$p = i^2 R_L = \left(\frac{V_{Th}}{R_{Th} + R_L} \right)^2 R_L$$

$$\begin{aligned} \frac{dp}{dR_L} &= V_{Th}^2 \left[\frac{(R_{Th} + R_L)^2 - 2R_L(R_{Th} + R_L)}{(R_{Th} + R_L)^4} \right] \\ &= V_{Th}^2 \left[\frac{(R_{Th} + R_L - 2R_L)}{(R_{Th} + R_L)^3} \right] = 0 \end{aligned}$$

$$0 = (R_{Th} + R_L - 2R_L) = (R_{Th} - R_L)$$

$$R_L = R_{Th}$$

$$p_{max} = \frac{V_{Th}^2}{4R_{Th}}$$

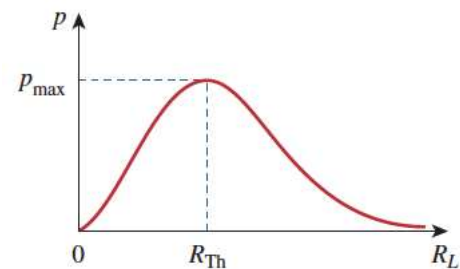


EHB 211E

22

22

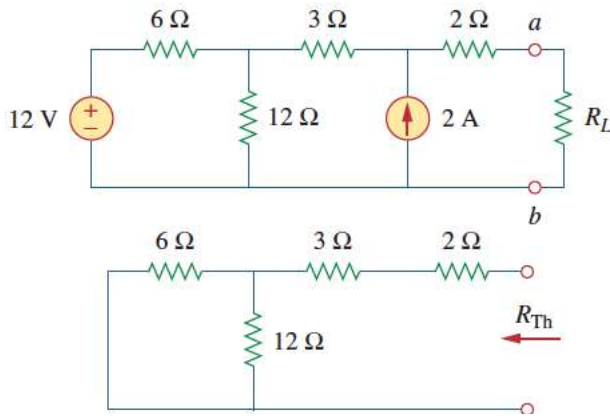
Exercise

Find the value of R_L for maximum power transfer



$$R_{Th} = 2 + 3 + 6 \parallel 12 = 5 + \frac{6 \times 12}{18} = 9 \Omega$$

$$R_L = R_{Th} = 9 \Omega$$

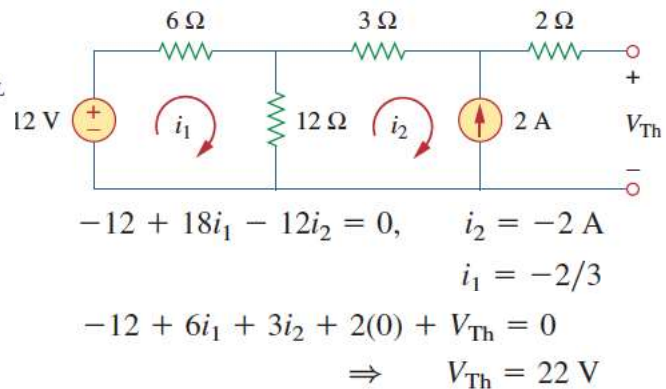


$$p_{\max} = \frac{V_{Th}^2}{4R_L} = \frac{22^2}{4 \times 9} = 13.44 \text{ W}$$

EHB 211E



23

23

Finding Thevenin equivalent using PSPICE

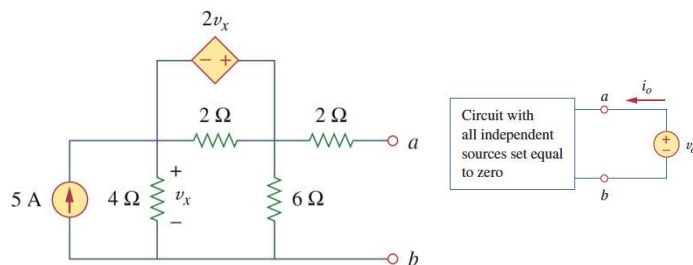

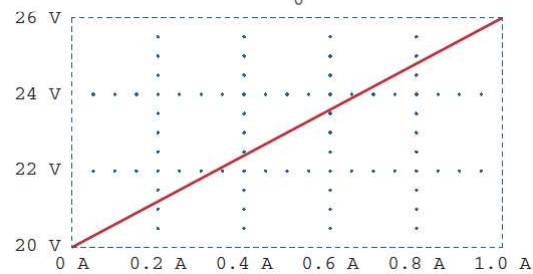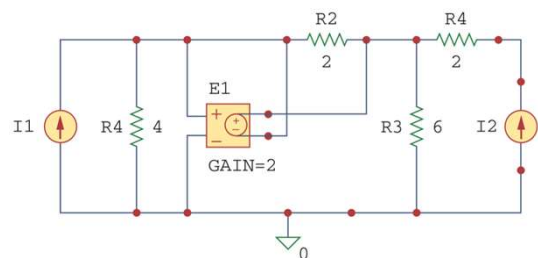Analysis/Setup DC Sweep
Sweep Type Linear
Sweep Var Current Source
Name I2
Start Value 0
End Value 1
Increment 0.1



$i_o = (v_o - v_{Th}) / R_{Th}$
-> 0 intercept of the below graph gives v_{Th}
-> slope gives R_{Th}

EHB 211E

24