

EHB 211E: Basics of Electrical Circuits

Operational Amplifiers

Asst. Prof. Ahmet Can Erten
(aerten@itu.edu.tr)

1

Motivation


- Two new and important passive elements will be introduced: capacitors & inductors
- Unlike resistors, which dissipate energy, capacitors and inductors store energy that can be retrieved at a later time. For this reason, these circuit elements are called *storage elements*.
- With capacitors and inductors, we will be able to analyze other practical circuits, that we can not using only resistors

31

Capacitors

- A capacitor is a passive element designed to store energy in its electric field.
- Besides resistors, capacitors are the most common electrical component.
- Capacitors are extensively used in electronics, communications, computers, and power systems.
- As an example, capacitors are used in tuning circuits of the radio receivers.

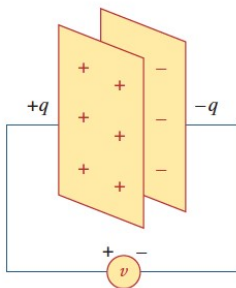A capacitor consists of two conducting plates separated by an insulator (or dielectric)



- When a voltage source is applied to the capacitor, the source deposits a positive charge on one plate and negative charge on the other.
- Therefore, the capacitor *stores* the electric charge.
- The amount of charge stored is proportional to the voltage:

$$q = Cv$$

32

32

Capacitors

$$q = Cv$$


Capacitance is the ratio of the charge on one plate of the capacitor to the voltage difference between two plates, measured in farads (F). 1 farad = 1 coulomb/volt.

- Capacitance does not depend on q or v . For the parallel plate capacitor:

$$C = \frac{\epsilon A}{d}$$

(A is the surface area, d is the distance between plates, and ϵ is the permittivity of the dielectric material between the plates)

- Typically capacitors have values in the pF (picofarad)- μ F (microfarad) range.

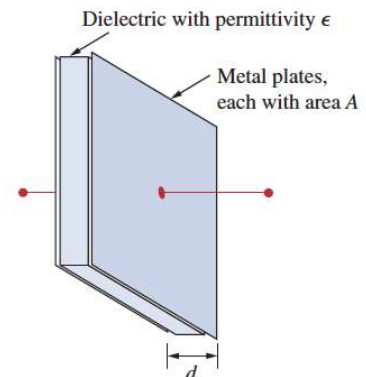


EHB 211E

33

33

Capacitors

- Circuit symbol

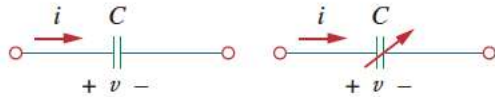

- If $v > 0$ and $i > 0$, or if $v < 0$ and $i < 0$, the capacitor is being charged.
- If $v \cdot i < 0$ the capacitor is discharging



Polyester,



ceramic

and



electrolytic capacitor



(a)



(b)

Variable capacitors
(trimmer and filmtrimmer type)

EHB 211E

34


34

Capacitors – current vs. voltage relationship

$$q = Cv \rightarrow i = \frac{dq}{dt} \rightarrow i = C \frac{dv}{dt}$$

$$i = C \frac{dv}{dt} \rightarrow v(t) = \frac{1}{C} \int_{-\infty}^t i(\tau) d\tau$$
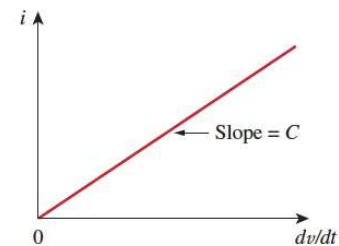
$$v(t) = \frac{1}{C} \int_{t_0}^t i(\tau) d\tau + v(t_0)$$



- Capacitor voltage depends on the past history of the capacitor current. Therefore capacitor has a memory!

EHB 211E

35

35

Capacitors – power and energy

Instantaneous power: $p = vi = Cv \frac{dv}{dt}$

Energy stored: $w = \int_{-\infty}^t p(\tau) d\tau = C \int_{-\infty}^t v \frac{dv}{d\tau} d\tau = C \int_{v(-\infty)}^{v(t)} v dv = \frac{1}{2} C v^2 \Big|_{v(-\infty)}^{v(t)}$

$v(-\infty) = 0 \rightarrow$ capacitor is uncharged at $t = -\infty$

$$\boxed{w = \frac{1}{2} C v^2} \quad \rightarrow \quad \boxed{q = C v} \quad \rightarrow \quad w = \frac{q^2}{2C}$$

EHB 211E

36

36

Capacitors – two important characteristics

- When the voltage across a capacitor is not changing with time
 \rightarrow the current through the capacitor is 0.
 \rightarrow **A capacitor is open to DC!**
- **The voltage on a capacitor cannot change abruptly**
 \rightarrow The voltage must be continuous in time
 (discontinuous change requires infinite current)

$$\boxed{i = C \frac{dv}{dt}}$$

EHB 211E

37

37


Exercise

Determine the current through a $200 \mu\text{F}$ capacitor, whose voltage characteristics is given as ->

$$v(t) = \begin{cases} 50t \text{ V} & 0 < t < 1 \\ 100 - 50t \text{ V} & 1 < t < 3 \\ -200 + 50t \text{ V} & 3 < t < 4 \\ 0 & \text{otherwise} \end{cases}$$

$$i(t) = \begin{cases} 10 \text{ mA} & 0 < t < 1 \\ -10 \text{ mA} & 1 < t < 3 \\ 10 \text{ mA} & 3 < t < 4 \\ 0 & \text{otherwise} \end{cases}$$

EHB 211E

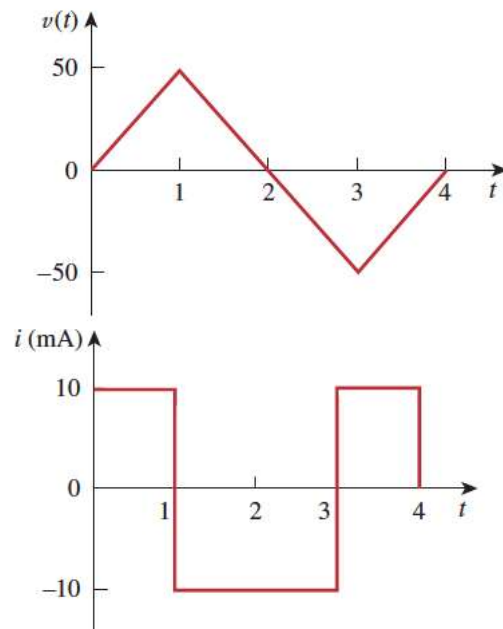

38

Exercise

Obtain the energy stored in each capacitor under DC conditions


$$i = \frac{3}{3 + 2 + 4}(6 \text{ mA}) = 2 \text{ mA}$$

$$v_1 = 2000i = 4 \text{ V} \quad v_2 = 4000i = 8 \text{ V}$$


$$w_1 = \frac{1}{2}C_1v_1^2 = \frac{1}{2}(2 \times 10^{-3})(4)^2 = 16 \text{ mJ}$$

$$w_2 = \frac{1}{2}C_2v_2^2 = \frac{1}{2}(4 \times 10^{-3})(8)^2 = 128 \text{ mJ}$$

EHB 211E

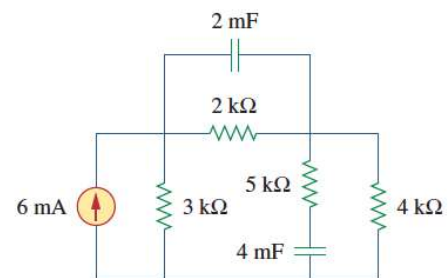

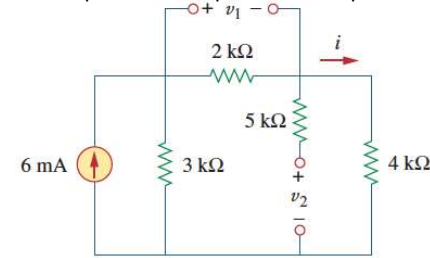-> Replace each capacitor with open circuit!



39

Capacitors – Series and Parallel Connection


Capacitors in parallel:

$$i = i_1 + i_2 + i_3 + \cdots + i_N$$

$$i = C_1 \frac{dv}{dt} + C_2 \frac{dv}{dt} + C_3 \frac{dv}{dt} + \cdots + C_N \frac{dv}{dt}$$

$$= \left(\sum_{k=1}^N C_k \right) \frac{dv}{dt} = C_{eq} \frac{dv}{dt}$$
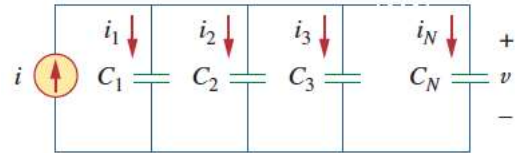
$$C_{eq} = C_1 + C_2 + C_3 + \cdots + C_N$$



Capacitors in parallel combine in a similar manner as conductance in parallel (or resistors in series)

EHB 211E

40

40

Capacitors – Series and Parallel Connection

Capacitors in series:

$$v = v_1 + v_2 + v_3 + \cdots + v_N$$

$$v_k = \frac{1}{C_k} \int_{t_0}^t i(\tau) d\tau + v_k(t_0)$$


$$v = \frac{1}{C_1} \int_{t_0}^t i(\tau) d\tau + v_1(t_0) + \frac{1}{C_2} \int_{t_0}^t i(\tau) d\tau + v_2(t_0)$$

$$+ \cdots + \frac{1}{C_N} \int_{t_0}^t i(\tau) d\tau + v_N(t_0)$$

$$= \left(\frac{1}{C_1} + \frac{1}{C_2} + \cdots + \frac{1}{C_N} \right) \int_{t_0}^t i(\tau) d\tau + v_1(t_0) + v_2(t_0)$$

$$+ \cdots + v_N(t_0)$$
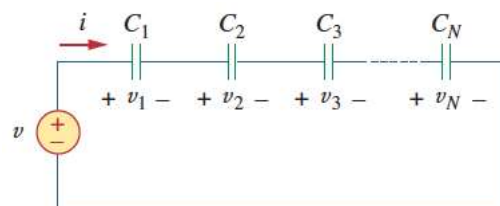
$$= \frac{1}{C_{eq}} \int_{t_0}^t i(\tau) d\tau + v(t_0)$$



$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} + \cdots + \frac{1}{C_N}$$

$$v(t_0) = v_1(t_0) + v_2(t_0) + \cdots + v_N(t_0)$$

Capacitors in series combine in a similar manner as resistors in parallel


EHB 211E

41

41

Inductors

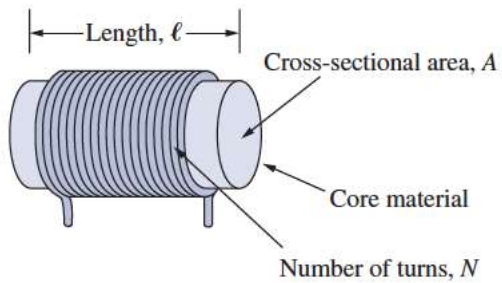An inductor is a passive element designed to store energy in its magnetic field.
An inductor consists of a coil of conducting wire



If a current is allowed to pass through an inductor, it is found that the voltage across the inductor is directly proportional to the time rate of change of the current:

$$v = L \frac{di}{dt}$$


L : inductance (units of Henry: $H = 1 \text{ volt} \cdot \text{second} / \text{ampere}$)

EHB 211E

42

42

Inductors

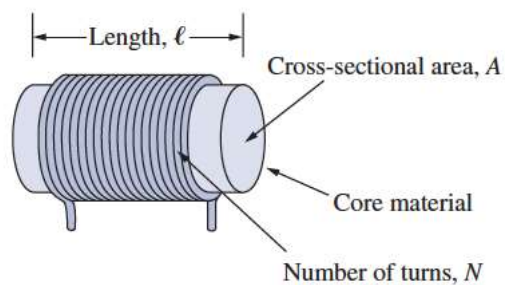

Inductance depends on physical dimensions and construction.

$$L = \frac{N^2 \mu A}{\ell}$$

N : number of turns

μ : permeability

A : cross-sectional area

L : length

EHB 211E

43

43

Inductors - types



(a) solenoidal




(b) toroidal




(c) chip

Typically inductors have values in the μH (microHenry)


Circuit symbol

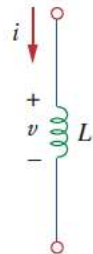

air-core

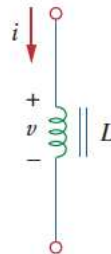

iron-core

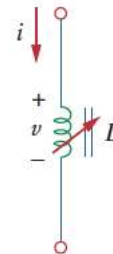

variable iron-core

EHB 211E

44


44

Inductors

$$v = L \frac{di}{dt}$$

$$di = \frac{1}{L} v dt \quad i = \frac{1}{L} \int_{-\infty}^t v(\tau) d\tau$$

$$i = \frac{1}{L} \int_{t_0}^t v(\tau) d\tau + i(t_0)$$

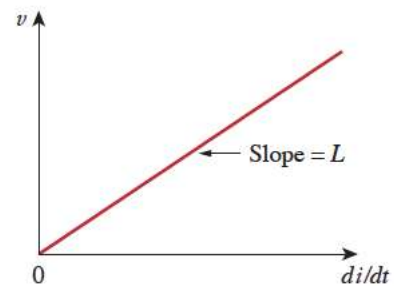


EHB 211E

45

45

Inductors – stored energy

$$v = L \frac{di}{dt}$$

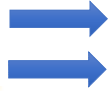

Inductor acts like a short circuit to DC !

The current through an inductor cannot change instantaneously

$$p = vi = \left(L \frac{di}{dt} \right) i$$

$$w = \int_{-\infty}^t p(\tau) d\tau = L \int_{-\infty}^t \frac{di}{d\tau} i d\tau$$

$$= L \int_{-\infty}^t i di = \frac{1}{2} Li^2(t) - \frac{1}{2} Li^2(-\infty)$$

$$i(-\infty) = 0 \rightarrow$$

$$w = \frac{1}{2} Li^2$$

EHB 211E

46

46

Exercise


Under DC conditions, find i , v_C and v_L . Also find the energy stored in the capacitor and the inductor.

$$i = i_L = \frac{12}{1 + 5} = 2 \text{ A}$$

$$v_C = 5i = 10 \text{ V}$$

$$w_C = \frac{1}{2} C v_C^2 = \frac{1}{2} (1)(10^2) = 50 \text{ J}$$

$$w_L = \frac{1}{2} L i_L^2 = \frac{1}{2} (2)(2^2) = 4 \text{ J}$$

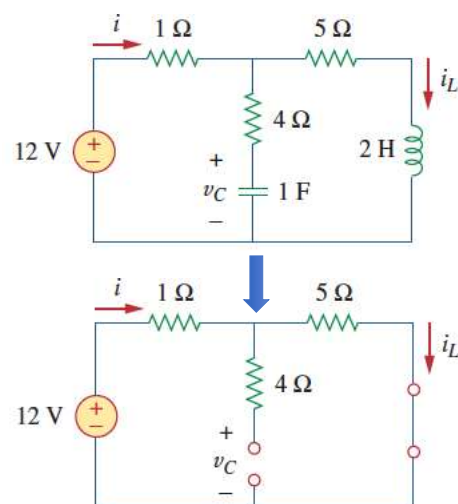

EHB 211E

47

47

Inductors – series connection

$$v = v_1 + v_2 + v_3 + \cdots + v_N$$


$$v = L_1 \frac{di}{dt} + L_2 \frac{di}{dt} + L_3 \frac{di}{dt} + \cdots + L_N \frac{di}{dt}$$

$$= (L_1 + L_2 + L_3 + \cdots + L_N) \frac{di}{dt}$$

$$= \left(\sum_{k=1}^N L_k \right) \frac{di}{dt} = L_{eq} \frac{di}{dt}$$

$$L_{eq} = L_1 + L_2 + L_3 + \cdots + L_N$$

(similar to series connection of resistors)

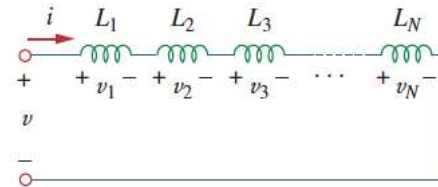

EHB 211E

48

48

Inductors – parallel connection

$$i = i_1 + i_2 + i_3 + \cdots + i_N$$

$$i = \frac{1}{L_1} \int_{t_0}^t v dt + i_1(t_0) + \frac{1}{L_2} \int_{t_0}^t v dt + i_2(t_0)$$

$$+ \cdots + \frac{1}{L_N} \int_{t_0}^t v dt + i_N(t_0)$$


$$= \left(\frac{1}{L_1} + \frac{1}{L_2} + \cdots + \frac{1}{L_N} \right) \int_{t_0}^t v dt + i_1(t_0) + i_2(t_0) + \cdots + i_N(t_0)$$

$$= \left(\sum_{k=1}^N \frac{1}{L_k} \right) \int_{t_0}^t v dt + \sum_{k=1}^N i_k(t_0) = \frac{1}{L_{eq}} \int_{t_0}^t v dt + i(t_0)$$

$$i(t_0) = i_1(t_0) + i_2(t_0) + \cdots + i_N(t_0)$$

$$\frac{1}{L_{eq}} = \frac{1}{L_1} + \frac{1}{L_2} + \frac{1}{L_3} + \cdots + \frac{1}{L_N}$$

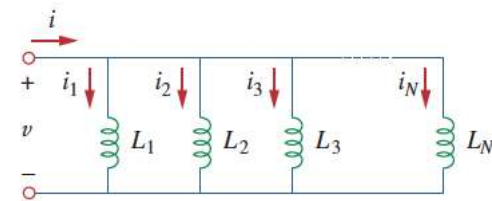(similar to parallel connection of resistors)



11E

49

49

Capacitors & Inductors: Summary

Relation	Resistor (R)	Capacitor (C)	Inductor (L)
$v-i$:	$v = iR$	$v = \frac{1}{C} \int_{t_0}^t i(\tau) d\tau + v(t_0)$	$v = L \frac{di}{dt}$
$i-v$:	$i = v/R$	$i = C \frac{dv}{dt}$	$i = \frac{1}{L} \int_{t_0}^t v(\tau) d\tau + i(t_0)$
p or w :	$p = i^2 R = \frac{v^2}{R}$	$w = \frac{1}{2} C v^2$	$w = \frac{1}{2} L i^2$
Series:	$R_{eq} = R_1 + R_2$	$C_{eq} = \frac{C_1 C_2}{C_1 + C_2}$	$L_{eq} = L_1 + L_2$
Parallel:	$R_{eq} = \frac{R_1 R_2}{R_1 + R_2}$	$C_{eq} = C_1 + C_2$	$L_{eq} = \frac{L_1 L_2}{L_1 + L_2}$
At dc:	Same	Open circuit	Short circuit
Circuit variable that cannot change abruptly:	Not applicable	v	i

EHB 211E

50

50

Exercise

For the circuit, $i(t) = 4(2 - e^{-10t})$ mA. If $i_2(0) = -1$ mA, find: $i_1(0)$, $v(t)$, $v_1(t)$, $v_2(t)$, $i_1(t)$, $i_2(t)$.

$$i(0) = 4(2 - 1) = 4 \text{ mA}$$

$$i_1(0) = i(0) - i_2(0) = 4 - (-1) = 5 \text{ mA}$$

$$L_{eq} = 2 + 4 \parallel 12 = 2 + 3 = 5 \text{ H}$$


$$v(t) = L_{eq} \frac{di}{dt} = 5(4)(-1)(-10)e^{-10t} \text{ mV} = 200e^{-10t} \text{ mV}$$

$$v_1(t) = 2 \frac{di}{dt} = 2(-4)(-10)e^{-10t} \text{ mV} = 80e^{-10t} \text{ mV}$$

$$v_2(t) = v(t) - v_1(t) = 120e^{-10t} \text{ mV}$$

$$\begin{aligned} i_1(t) &= \frac{1}{4} \int_0^t v_2 dt + i_1(0) = \frac{120}{4} \int_0^t e^{-10\tau} d\tau + 5 \text{ mA} \\ &= -3e^{-10\tau} \Big|_0^t + 5 \text{ mA} = -3e^{-10t} + 3 + 5 = 8 - 3e^{-10t} \text{ mA} \end{aligned}$$

$$\begin{aligned} i_2(t) &= \frac{1}{12} \int_0^t v_2 dt + i_2(0) = \frac{120}{12} \int_0^t e^{-10\tau} d\tau - 1 \text{ mA} \\ &= -e^{-10\tau} \Big|_0^t - 1 \text{ mA} = -e^{-10t} + 1 - 1 = -e^{-10t} \text{ mA} \end{aligned}$$

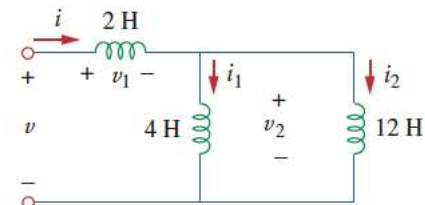

EHB 211E

51

51

Applications: Integrator

$$i_R = i_C$$

$$i_R = \frac{v_i}{R}, \quad i_C = -C \frac{dv_o}{dt}$$


$$\frac{v_i}{R} = -C \frac{dv_o}{dt}$$

$$dv_o = -\frac{1}{RC} v_i dt$$

$$v_o(t) - v_o(0) = -\frac{1}{RC} \int_0^t v_i(\tau) d\tau$$

$$v_o = -\frac{1}{RC} \int_0^t v_i(\tau) d\tau$$

Assuming the capacitor is discharged ($v_o(0) = 0$) prior to the application of the signal

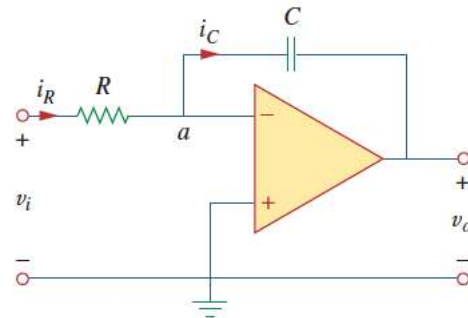

EHB 211E

52

52

Exercise

If $v_1(t) = 10\cos 2t$ mV, $v_2(t) = 0.5t$ mV, find $v_o(t)$.


The circuit is a summing integrator!

$$v_o = -\frac{1}{R_1 C} \int v_1 dt - \frac{1}{R_2 C} \int v_2 dt$$

$$= -\frac{1}{3 \times 10^6 \times 2 \times 10^{-6}} \int_0^t 10 \cos(2\tau) d\tau$$

$$- \frac{1}{100 \times 10^3 \times 2 \times 10^{-6}} \int_0^t 0.5\tau d\tau$$

$$= -\frac{1}{6} \frac{10}{2} \sin 2t - \frac{1}{0.2} \frac{0.5t^2}{2} = -0.833 \sin 2t - 1.25t^2 \text{ mV}$$

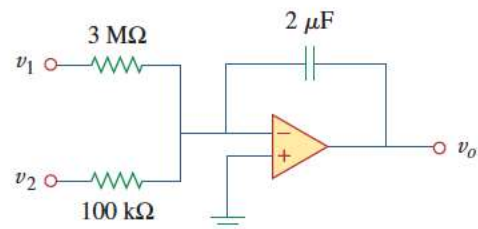

EHB 211E

53


53

Applications: Differentiator

$$i_R = i_C$$

$$i_R = -\frac{v_o}{R}, \quad i_C = C \frac{dv_i}{dt}$$

$$v_o = -RC \frac{dv_i}{dt}$$

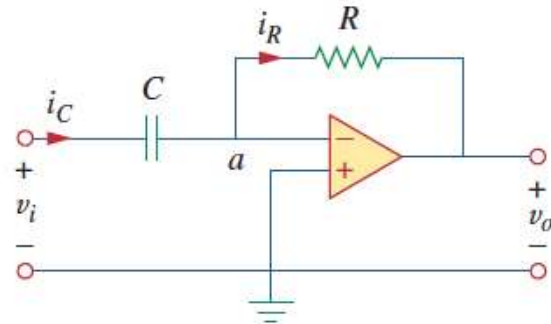

EHB 211E

54

54


Exercise

For the circuit, sketch the output for the given input

$$RC = 5 \times 10^3 \times 0.2 \times 10^{-6} = 10^{-3} \text{ s}$$

$$v_i = \begin{cases} 2000t & 0 < t < 2 \text{ ms} \\ 8 - 2000t & 2 < t < 4 \text{ ms} \end{cases}$$

$$v_o = -RC \frac{dv_i}{dt} = \begin{cases} -2 \text{ V} & 0 < t < 2 \text{ ms} \\ 2 \text{ V} & 2 < t < 4 \text{ ms} \end{cases}$$

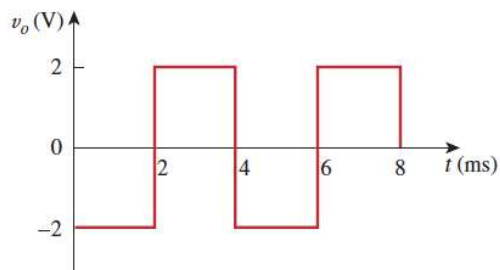

EHB 211E

55

55

